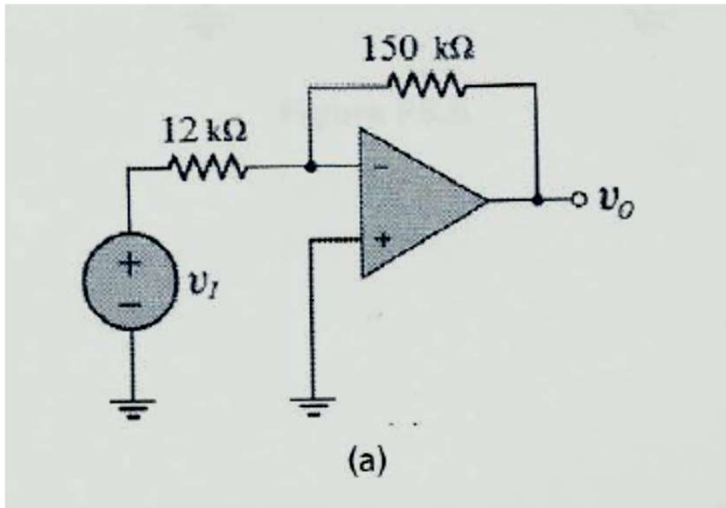


Operation Amplifier - Examples

Example: Inverting Amplifier




$$\text{Gain} = - (R_2 / R_1) = -(150/12) = \mathbf{-12.5}$$

Example 2: Inverting Amplifier

A voltage source V_S with source resistance $R_S = 1.5 \text{ k}\Omega$ is connected to the input of an op-amp inverting amplifier circuit

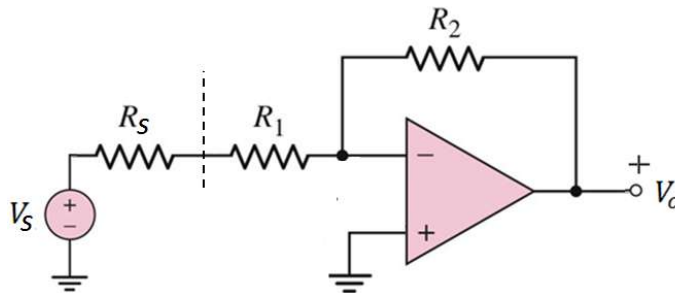- (a) If the $R_1 = 1.0 \text{ k}\Omega$ and $R_2 = 15.0 \text{ k}\Omega$, then calculate the voltage gain, V_O/V_S
- (b) Determine the output voltage V_O for the source voltage $V_S = 45 \text{ mV}$



Answers:


(a) - 6

(b) - 0.27 V

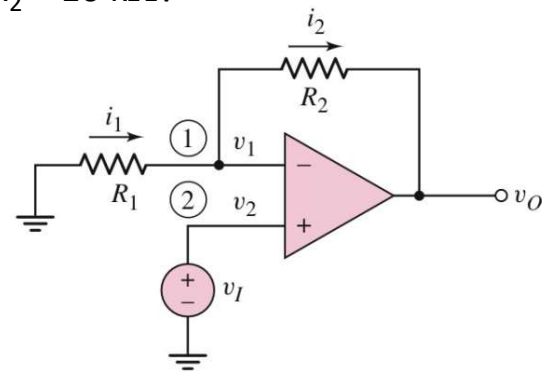Example 1: Non-Inverting Amplifier

What is the gain of the circuit when $R_1 = 1 \text{ k}\Omega$, $R_2 = 10 \text{ k}\Omega$?

$$A_v = 1 + \frac{R_2}{R_1}$$
$$A_v = 1 + \frac{R_2}{R_1} = 1 + \frac{10 \text{ k}\Omega}{1 \text{ k}\Omega} = 11$$




Noninverting amplifier

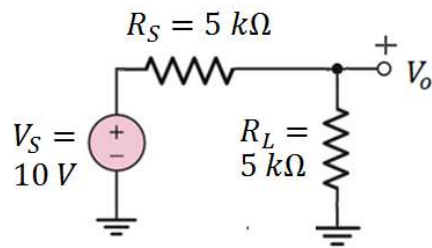
Example 1: Buffer Amplifier (Voltage Follower)

A voltage source V_S with source resistance $R_S = 5\text{ k}\Omega$ is connected to a load resistance input of $R_L = 5\text{ k}\Omega$ directly and through a buffer amplifier as shown in the figures below.

- Determine the output voltage across the load and the current in the resistance R_L for each circuit configuration



Load directly connected to the source

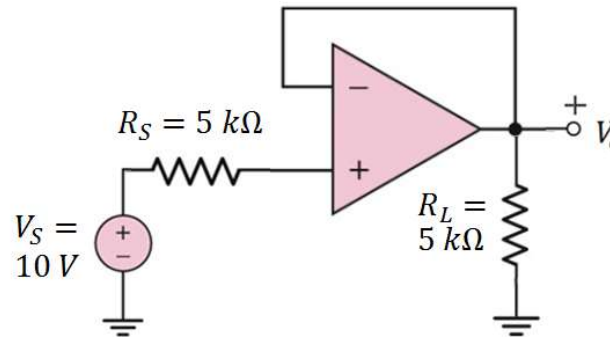

Load connected to the source via a buffer

Answers:

$V_o = 5\text{ V}$, Current = 1 mA

$V_o = 10\text{ V}$, current = 2 mA

Example 1: Summing Amplifier

Design a summing amplifier as shown in figure to produce a specific output signal, such that $v_o = 1.25 - 2.5 \cos \omega t$ volt. Assume the input signals are $v_{i1} = -1.0 \text{ V}$, $v_{i2} = 0.5 \cos \omega t$ volt. Assume the feedback resistance $R_F = 10 \text{ k}\Omega$

Solution: output voltage


$$v_o = -R_F \left(\frac{v_{I1}}{R_1} + \frac{v_{I2}}{R_2} + \frac{v_{I3}}{R_3} \right) = -R_F \left[\frac{(-1)}{R_1} + \frac{0.5 \cos \omega t}{R_2} \right]$$

$$\text{Or, } 1.25 - 2.5 \cos \omega t = R_F \left[\frac{1}{R_1} - \frac{0.5 \cos \omega t}{R_2} \right]$$

$$\text{Or, } \boxed{1.25} - \boxed{2.5 \cos \omega t} = \boxed{\frac{R_F}{R_1}} - \boxed{\left(\frac{R_F}{R_2} \right) (0.5 \cos \omega t)}$$

$$\frac{R_F}{R_1} = 1.25 \quad \text{or} \quad R_1 = \frac{R_F}{1.25} = \frac{10 \text{ k}\Omega}{1.25} = 8 \text{ k}\Omega$$

$$\frac{R_F}{R_2} (0.5 \cos(\omega t)) = 2.5 \cos(\omega t) \quad \text{or} \quad R_2 = R_F \frac{0.5 \cos(\omega t)}{2.5 \cos(\omega t)} = 10 \times \frac{0.5}{2.5} = 2 \text{ k}\Omega$$

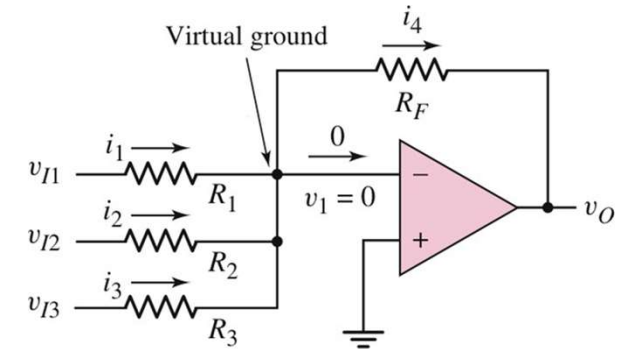

Example 1: Integrator

The integrator circuit as shown in figure has an initial voltage $V_x = -1.4$ V across the capacitor at time $t = 0$. A step input voltage $V_S = -2$ V is applied at time $t = 0$. Determine the RC time constant necessary such that the output voltage reaches $+10.2$ V at time $t = 5.0$ ms.


Solution: The output voltage

$$V_o = V_x - \frac{1}{R_1 C} \int V_S dt$$

$$= V_x - \frac{1}{R_1 C} \int_0^5 V_S dt$$

$$10.2 = -1.4 - \frac{(-2)}{R_1 C} \int_0^5 dt = -1.4 + \frac{2}{R_1 C} [5 - 0]$$

$$R_1 C = 0.862 \text{ ms}$$

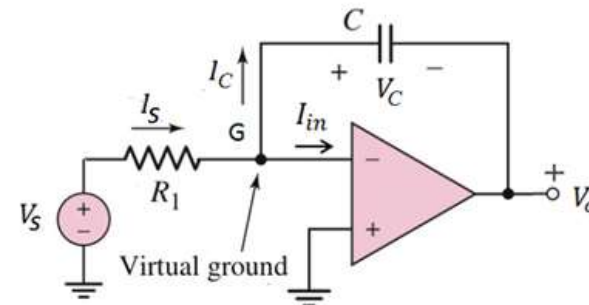

Example 1: Differentiator

Determine the output voltage of a differentiator circuit. Assume that the input voltage $v_I = 3.5\cos(100\pi t)$ V and the time constant $R_2C_1 = 1.5$ ms.


Solution:

The output voltage

$$v_O = -R_2C_1 \frac{dv_I}{dt}$$
$$= -(1.5 \times 10^{-3}) \frac{d[3.5 \cos(100\pi t)]}{dt}$$


$$v_O = -(1.5 \times 10^{-3})[-3.5 \times 100\pi \times \sin(100\pi t)]$$

$$v_O = 1.65 \sin(100\pi t) \text{ volt}$$

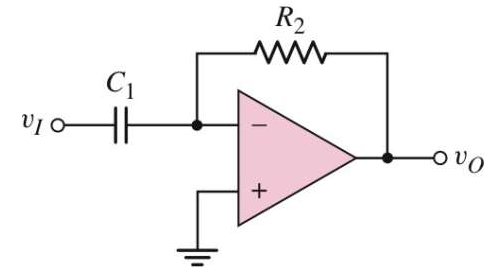

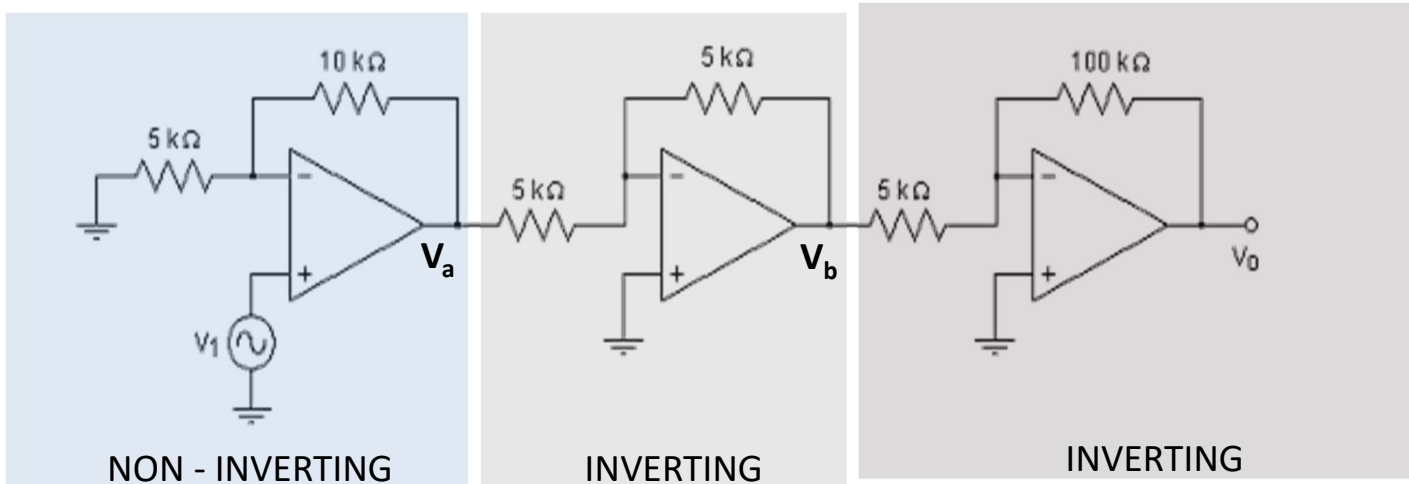Example 1: Multi-Stage Amplifier

Calculate the input voltage if the final output, V_o is 10.08 V.



Finally:

$$V_a = \left(1 + \frac{10k\Omega}{5k\Omega}\right) V_1$$

$$0.504 = 3V_1$$

$$V_1 = 0.168V$$



Then:

$$V_b = -\frac{5}{5} V_a$$

$$-0.504 = -V_a$$

$$V_a = 0.504V$$




Need to work backward:

$$V_o = -\frac{100k\Omega}{5k\Omega} V_b$$

$$10.08 = -20V_b$$

$$V_b = -0.504V$$

Example 2: Multi-Stage Amplifier

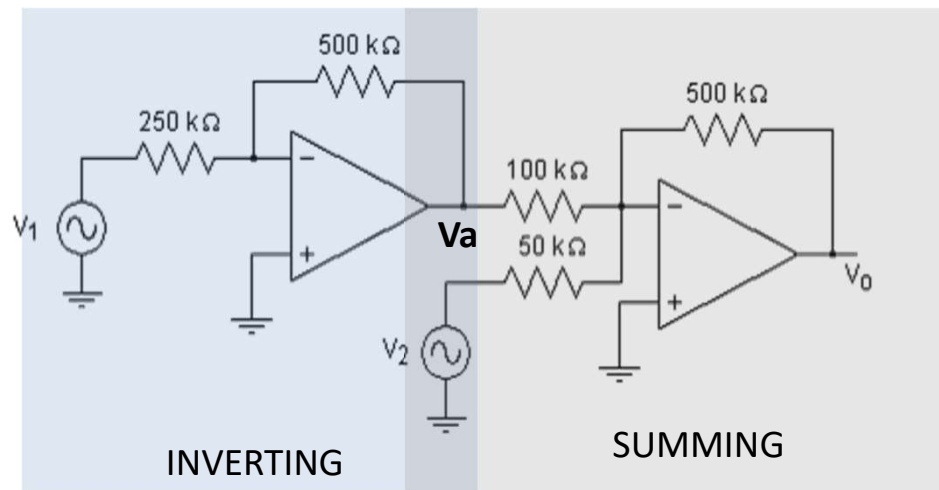

Calculate the output voltage, V_0 if $V_1 = V_2 = 700$ mV

$$V_a = -(500/250) 0.7$$
$$V_a = -1.4 \text{ V}$$



Then:

$$V_0 = -500 [V_a / 100 + V_2 / 50]$$
$$V_0 = -500 [-1.4 / 100 + 0.7 / 50]$$
$$V_0 = 0 \text{ V}$$

Calculating Gain and Design Questions

INVERTING

Voltage gain, $A_v = \frac{V_0}{V_i} = -\frac{R_2}{R_1}$

NON - INVERTING

Voltage gain, $A_v = \frac{V_0}{V_i} = 1 + \frac{R_2}{R_1}$

Calculating Output and Design Questions

SUMMING AMPLIFIER

Output voltage

$$V_0 = -R_F \left(\frac{V_{i1}}{R_1} + \frac{V_{i2}}{R_2} + \frac{V_{i3}}{R_3} \right)$$

DIFFERENTIATOR AMPLIFIER

Output voltage, $v_0 = -R_2 C_1 \frac{dv_I}{dt}$


INTEGRATOR AMPLIFIER

Output voltage, $v_0 = -\frac{1}{R_1 C_2} \int v_I dt$

If the capacitor has some initially voltage, V_C

$$v_0 = V_C - \frac{1}{R_1 C_2} \int v_I dt$$

Example 3:

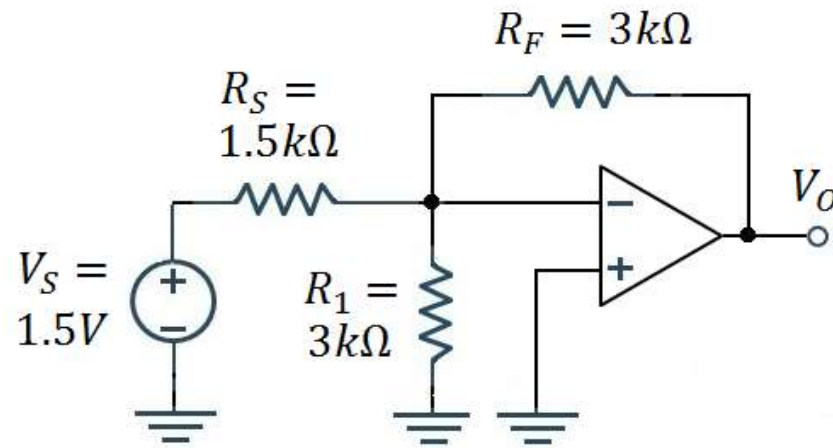

Calculate the output voltage V_O of the operational amplifier circuit as shown in the figure.

Answer: -3 V