
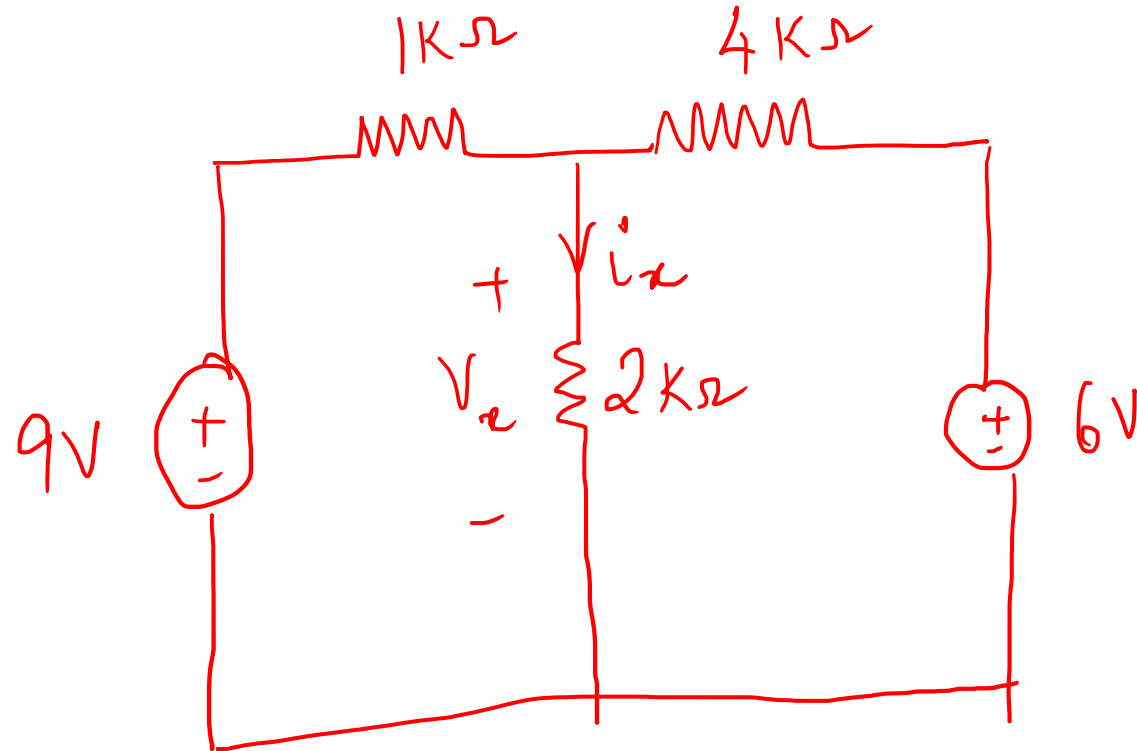


For the circuit given below, determine the current flowing through and voltage across the $2\text{k}\Omega$ resistor using the following methods

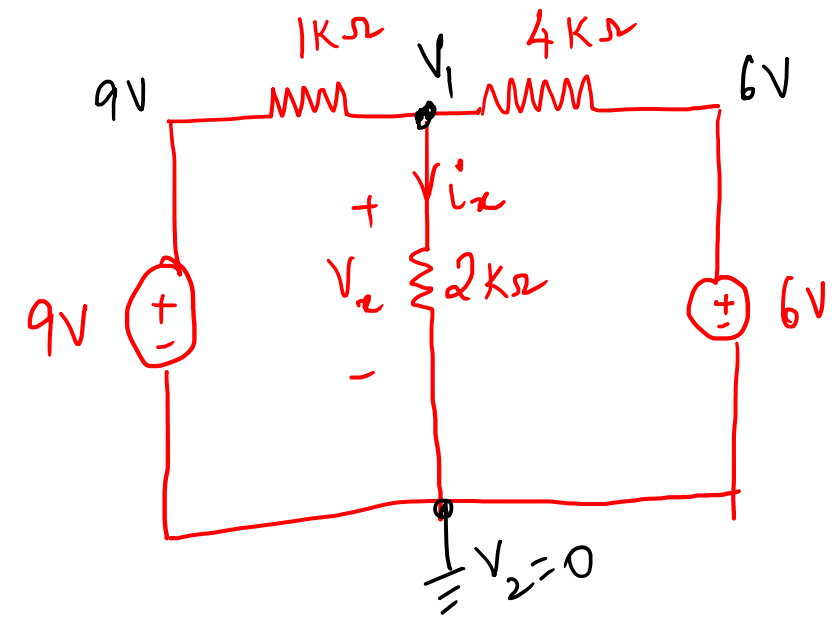- Nodal analysis
- Mesh analysis
- Thevenin's theorem
- Norton's theorem
- Superposition theorem
- Source transformation






Nodal Analysis

$$\frac{V_1 - 9}{1\text{k}} + \frac{V_1 - 0}{2\text{k}} + \frac{V_1 - 6}{4\text{k}} = 0$$

$$\underline{V_1 = 6\text{V}}$$

$$i_2 = \frac{V_1}{2\text{k}} = \frac{6\text{V}}{2\text{k}} = \underline{3\text{mA}}$$

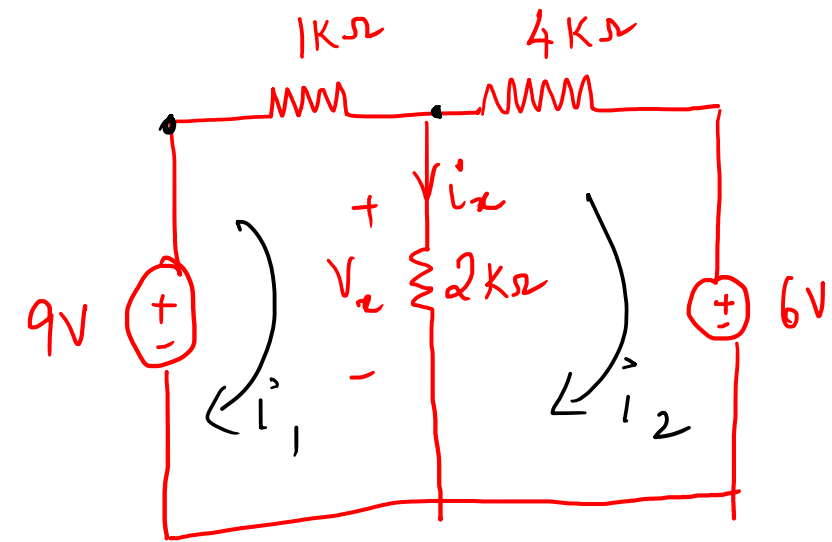

Mesh 1:

$$i_1(1K) + 2K(i_1 - i_2) - 9 = 0$$

$$3i_1 - 2i_2 = 9 \quad - \textcircled{1}$$

Mesh 2:

$$4K(i_2) + 6 + 2K(i_2 - i_1) = 0$$

$$-2i_1 + 6i_2 = -6 \quad - \textcircled{2}$$

Solving Eqn $\textcircled{1}$ & $\textcircled{2}$



$$i_1 = 3\text{mA}$$

$$i_x = i_1 - i_2 = \underline{3\text{mA}}$$

$$i_2 = 0$$

$$\underline{V_{2K} = 6V}$$

Thevenin's Theorem

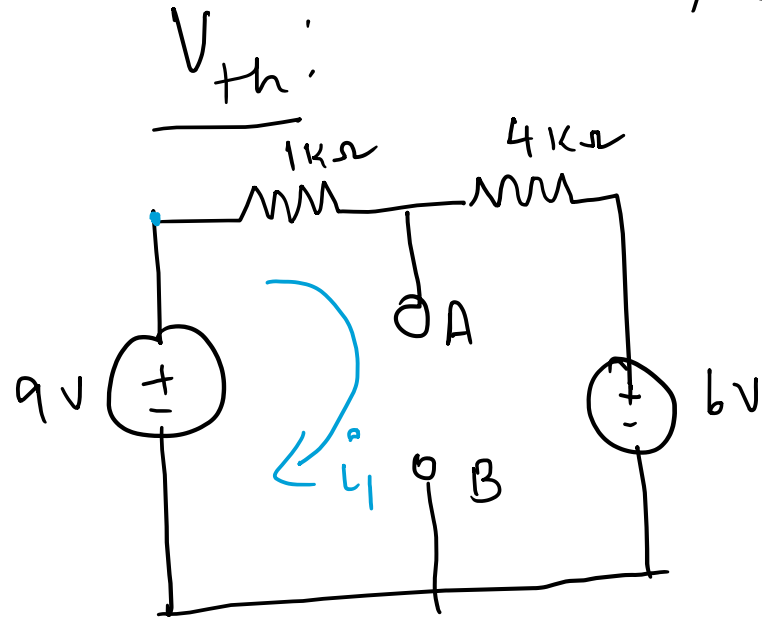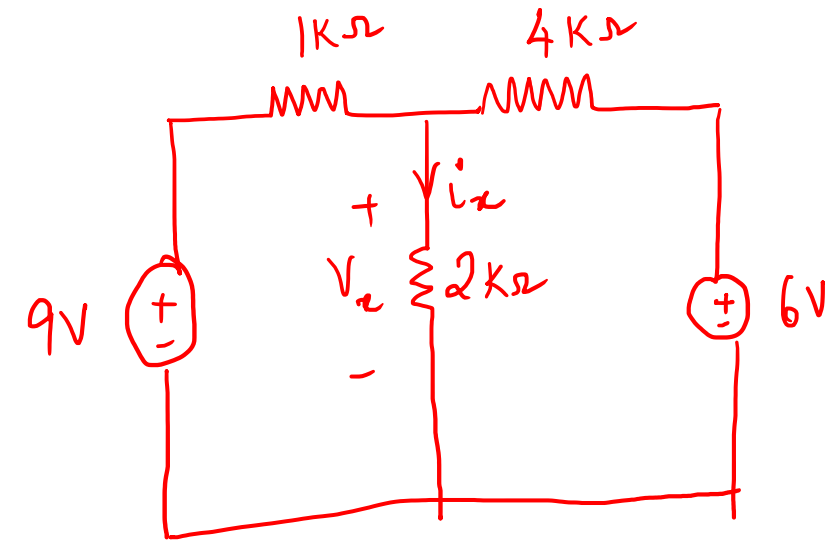


$$i_1(1k) + V_{AB} - 9 = 0$$

$$V_{AB} = 9 - 1k(i_1)$$

$$= \underline{8.4V}$$


R_{th} :


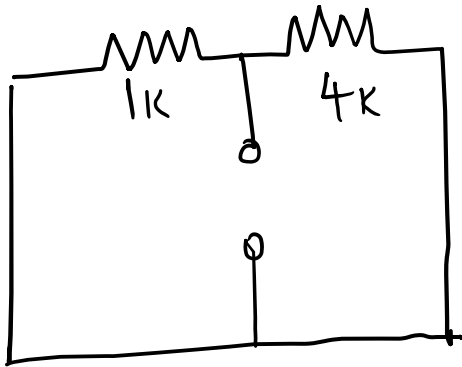


$$R_{th} = \frac{1 \parallel 4}{1} = 0.8k\Omega$$

$$i_1 = \frac{9-6}{1+4} = \frac{3}{5} = 0.6mA$$

$$R_{th} = 0.8k\Omega$$

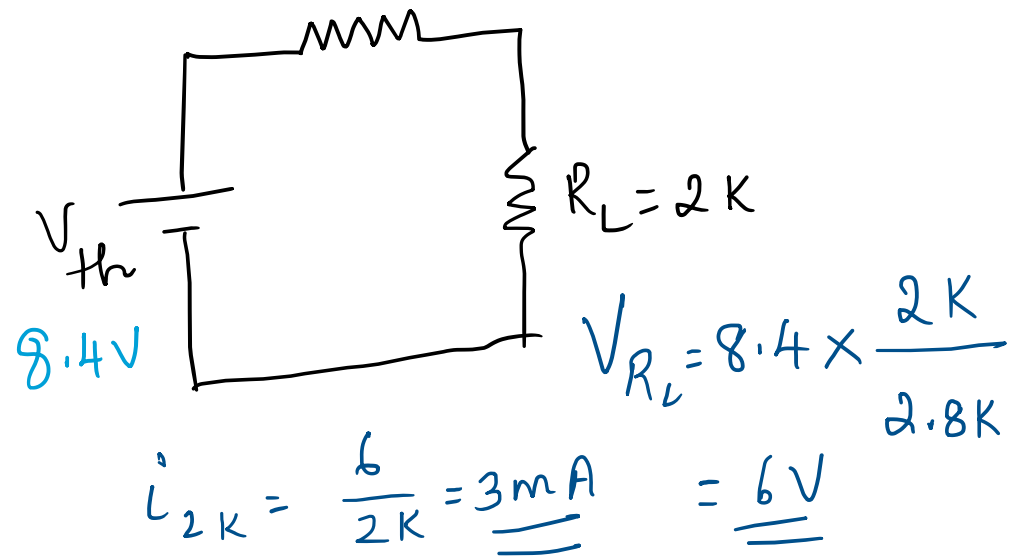

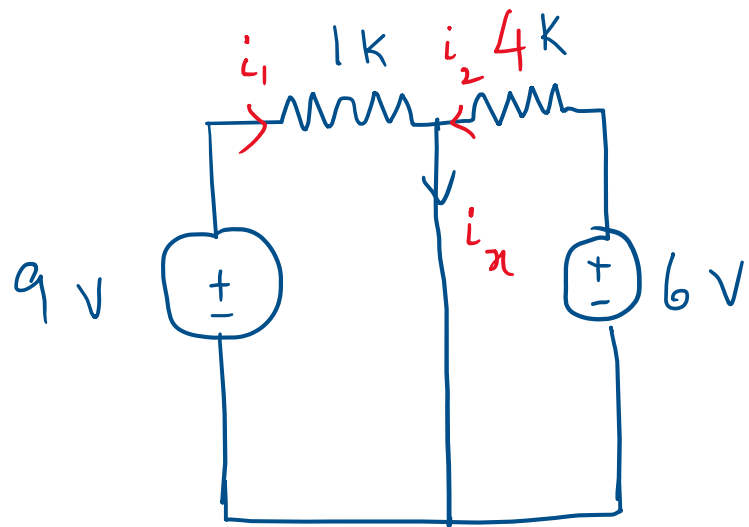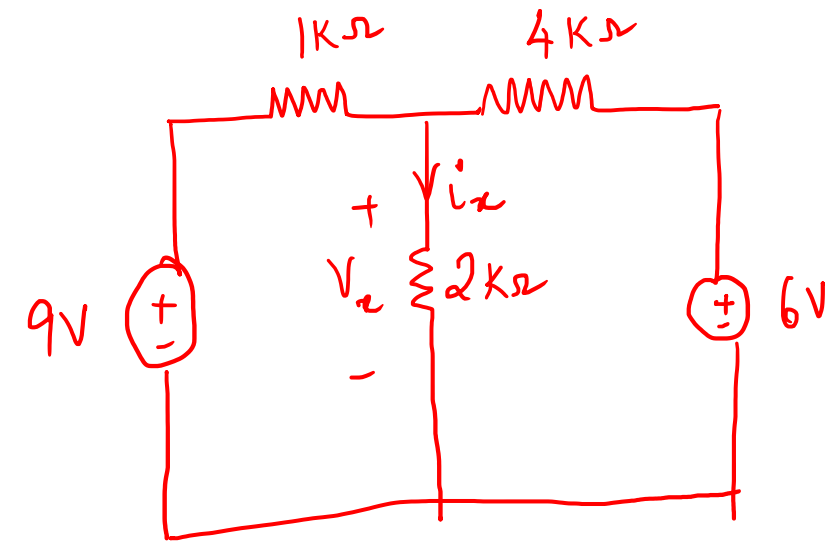

Norton's theorem

$$i_x = i_1 + i_2$$

$$= \frac{9}{1k} + \frac{6}{4k}$$

$$= (9 + 1.5) = \underline{10.5mA}$$

$$R_N = R_{th} = 0.8k\Omega$$


(Solved in
Previous slide)


$$V_{2k} = 3mA \times 2k\Omega$$

$$\underline{V_{2k} = 6V}$$

$$i_{R_L} = 10.5 \times \frac{0.8}{2.8}$$


$$i_{2k} = \underline{3mA}$$

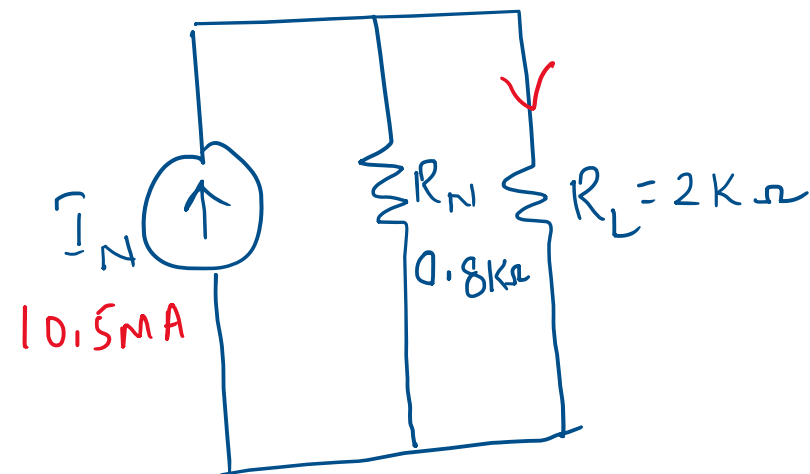

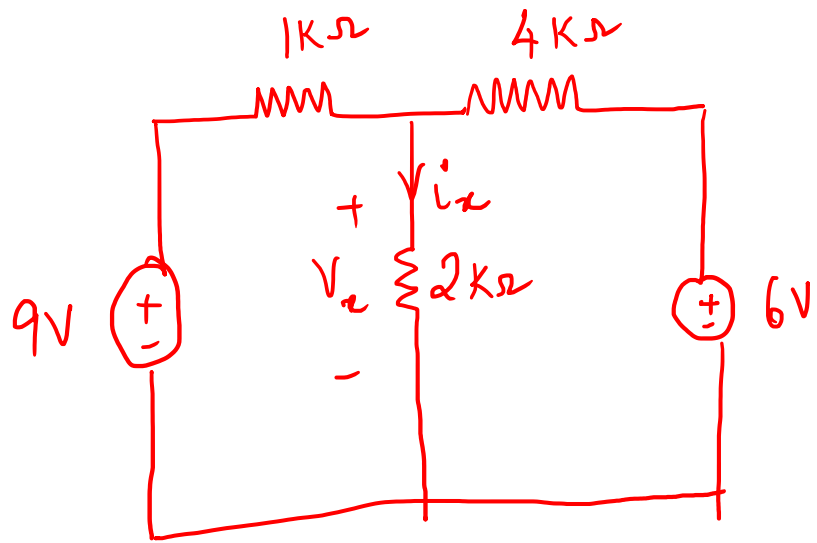


\Rightarrow

Source Transformation

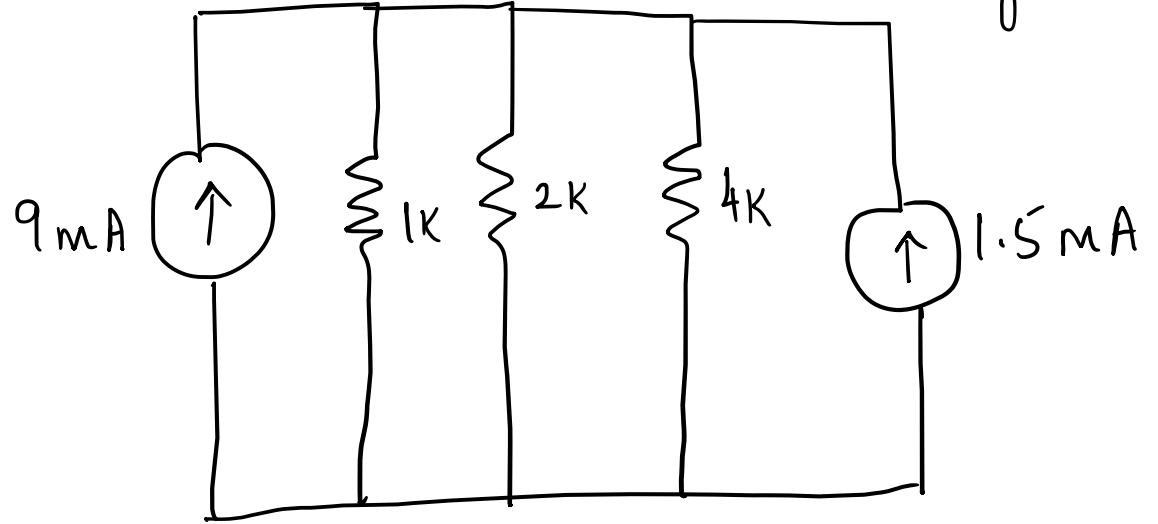

\Downarrow

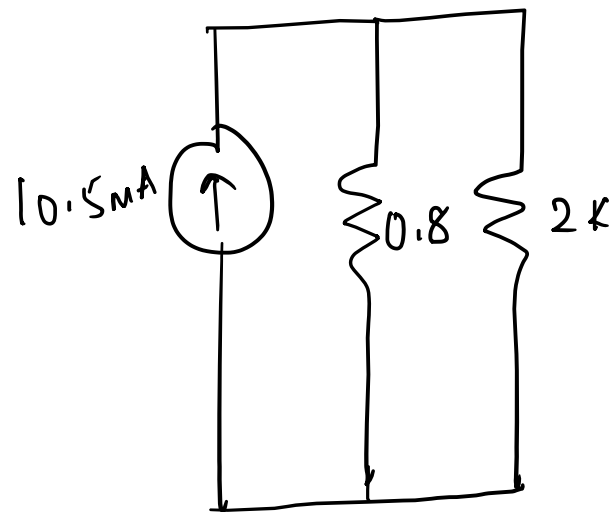


$$i_{2k} = 10.5 \times \frac{0.8}{2.8}$$

$$= \underline{3 \text{ mA}}$$


$$V_{2k} = 3 \text{ mA} \times 2 \text{ k}$$

$$= \underline{6 \text{ V}}$$

Superposition Theorem

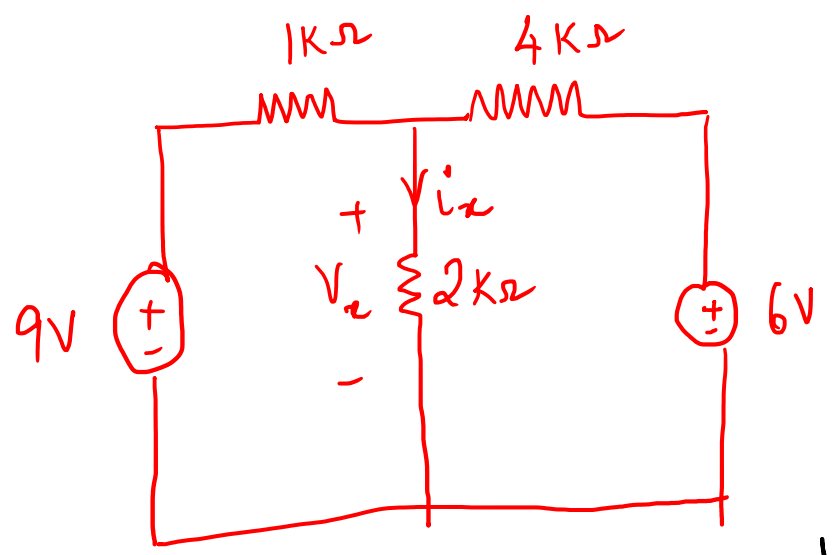

Consider 9V source

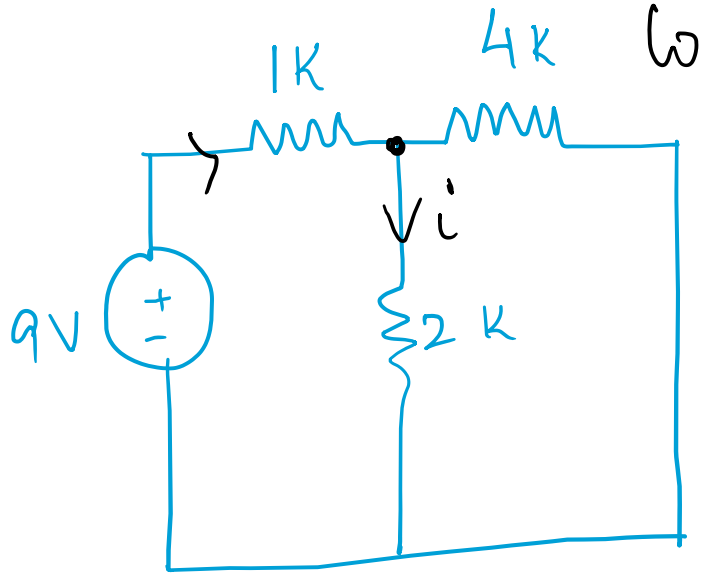

$$i_{2k} = 3.86 \times \frac{4}{2+4}$$


$$i_{2k}^{(1)} = \underline{2.57 \text{ mA}}$$

$$i_{tot} = \frac{9}{1+(2||4)} = 3.86 \text{ mA}$$

$$i_{2k} = i^{(1)} + i^{(2)}$$

$$V_{2k} = 3 \times 2 = \underline{6V} = 2.57 + 0.43 = \underline{\underline{3 \text{ mA}}}$$

Consider 6V source

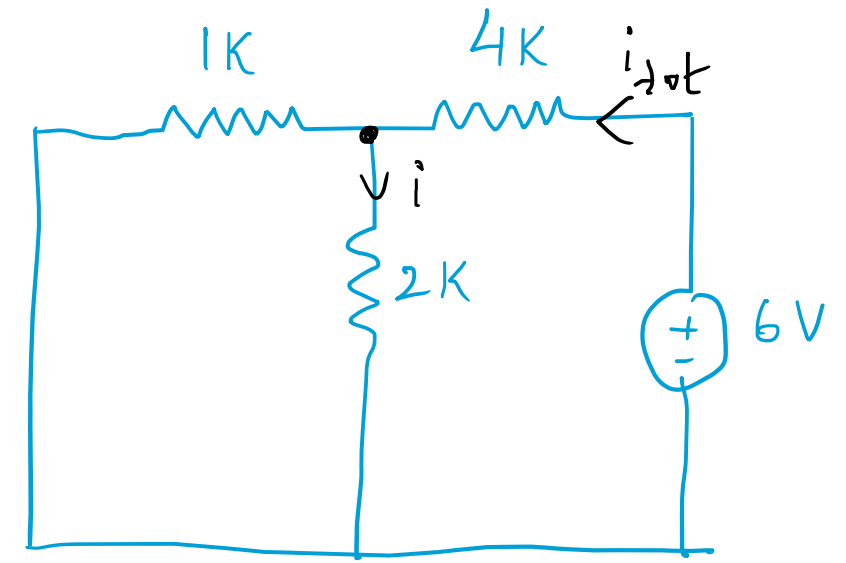

$$i_{tot} = \frac{6}{4+(2||1)} = 1.28 \text{ mA}$$

$$i_{2k}^{(2)} = 1.28 \times \frac{1k}{3k} = 0.43 \text{ mA}$$