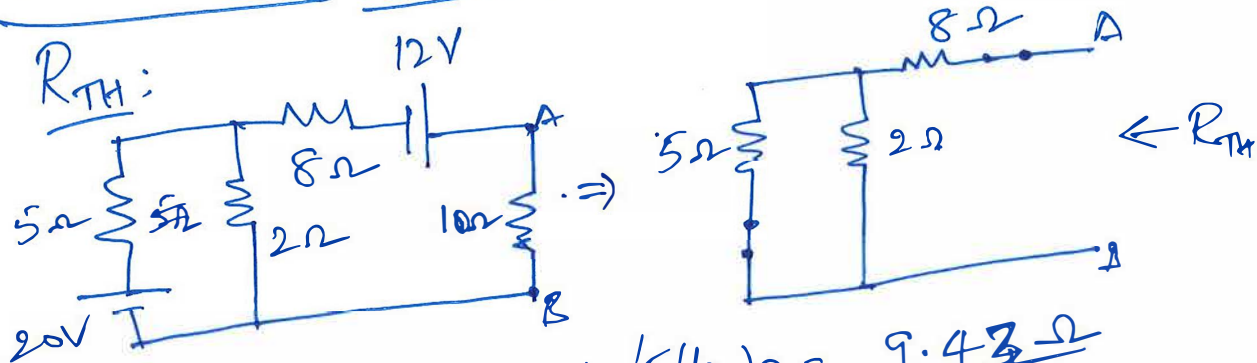


SOLUTIONS


1 & 2

Fig. 1


Thevenin's Equivalent:


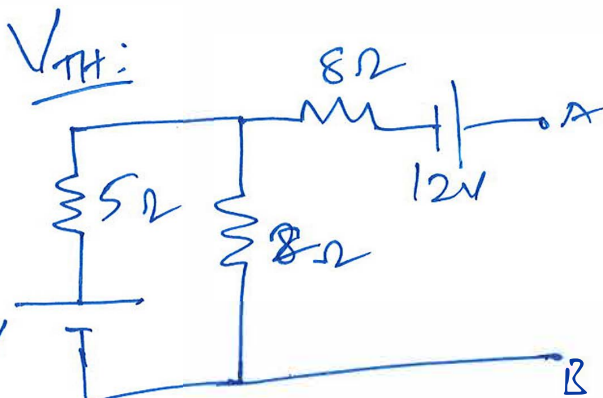
$$R_{TH} = 8\Omega + (5 \parallel 2)\Omega = 9.43\Omega$$



Using source transformation

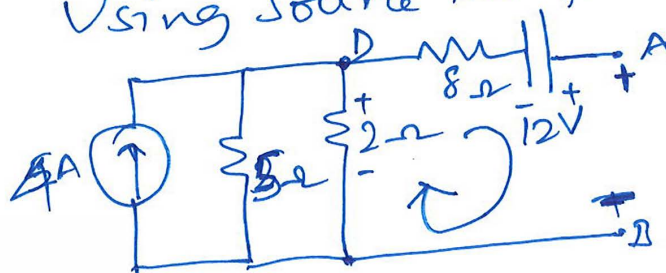



$$I_{2\Omega} = \frac{4 \times 5}{2 + 5} = 2.86A$$

Apply KVL in loop ABDA $12 + V_{AB} + 2 \times 2.86 = 0$
 $V_{AB} = +17.714V = V_{TH}$

$$V_{TH} = V_{AB} = +17.714V$$

Equivalent circuit:

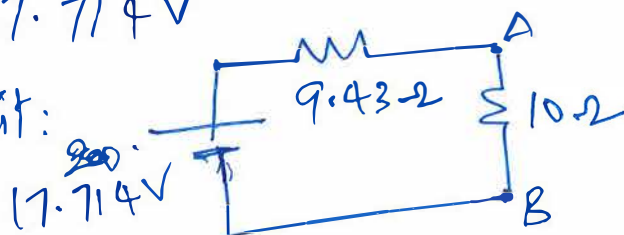

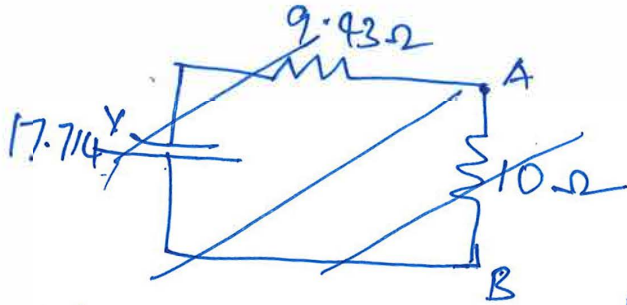

$$I_L = \frac{17.714}{9.43 + 10} = 911.7 \text{ mA}$$

$$V_L = \frac{17.714 \times 10}{19.43} = 9.117 \text{ V}$$

$$P_L = V_L \cdot I_L = 8.31 \text{ W}$$

As $R_L \neq R_{TH}$, maximum power is transferred.

Maximum power is transferred when $R_L = R_{TH}$


$$P_{max} = V_L \Big|_{R_L=R_{TH}} \cdot I_L \Big|_{R_L=R_{TH}} = \frac{V_{TH}}{2} \cdot \frac{V_{TH}}{2R_{TH}} = \frac{V_{TH}^2}{4R_{TH}}$$

$$P_{max} = 8.32 \text{ W}$$

Norton Equivalent


$$R_N = R_{TH} = 9.43 \Omega$$

to find I_N :

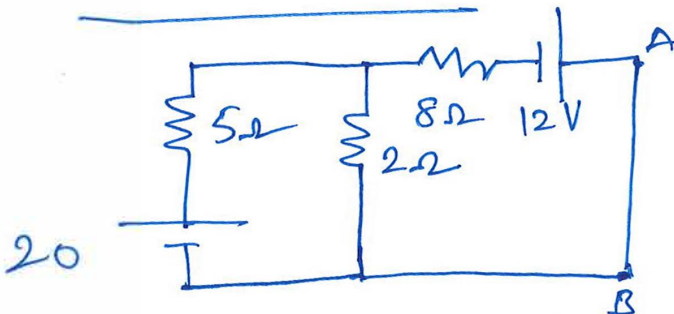

Using source transformation,


$$I_s = \frac{20}{5} = 4 \text{ A}$$

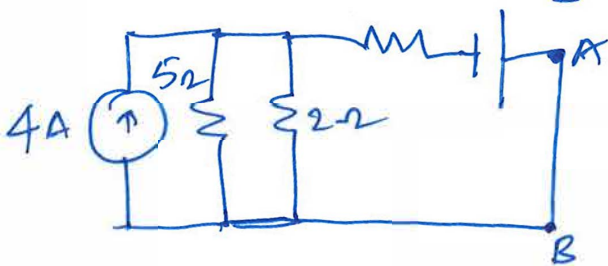

$$5 // 2 = 1.43 \Omega$$


Using source transformation

$$V_s = 4 \times 1.43 = 5.72 \text{ V}$$

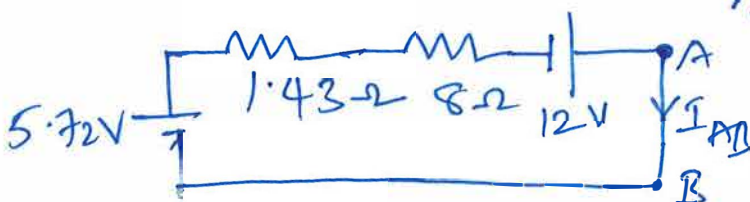

$$I_{AB} = \frac{12 + 5.72}{1.43 + 8} = 1.88 \text{ A}$$

$$I_N = I_{AB} = 1.88 \text{ A}$$

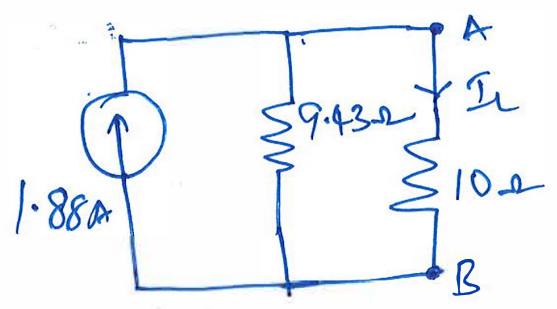


$$I_L = \frac{1.88 \times 9.43}{10 + 9.43} \approx 912 \text{ mA}$$

$$V_L = 9.12 \text{ V}$$



$$P_L = I_L \cdot V_L = \underline{8.32 \text{ W}}$$

(small errors are due to rounding off)


Fig. 2

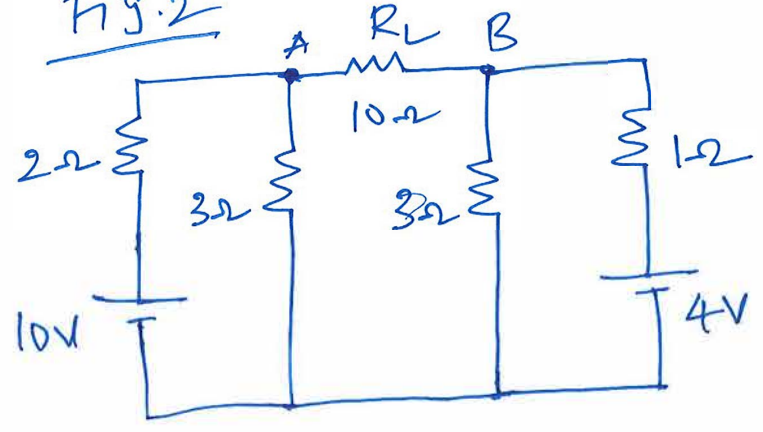

THEVENIN'S EQUIVALENT:

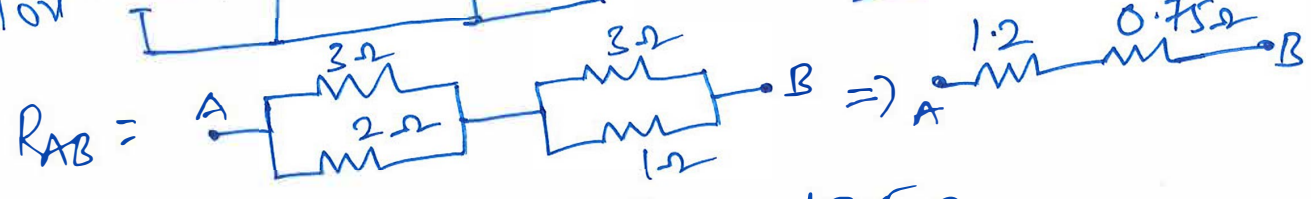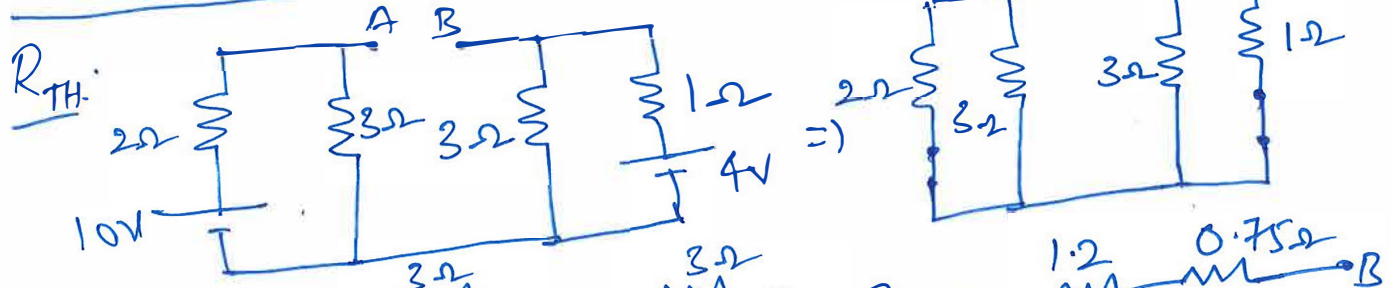
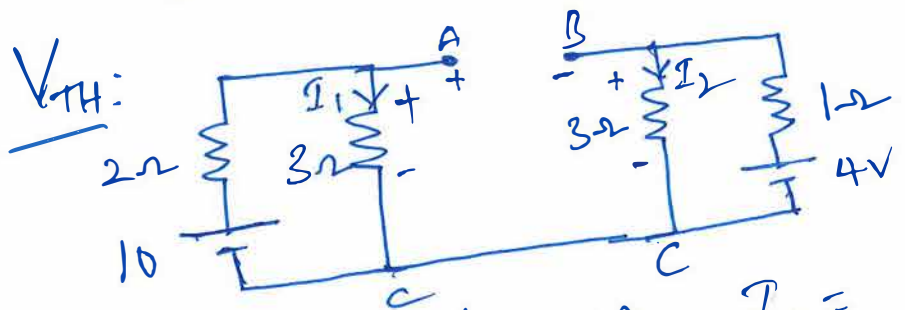
$$R_{AB} = 1.95 \Omega \quad R_{TH} = R_{AB} = 1.95 \Omega$$



$$I_1 = \frac{10}{5} = 2 \text{ A} \quad I_2 = \frac{4}{4} = 1 \text{ A}$$

Applying KVL in the loop ABCA,

$$V_{AB} = 3 \times 2 - 3 \times 1 = 3V$$

$$V_{TH} = V_{AB} = \underline{3V}$$



$$V_L = \frac{3 \times 10}{10 + 1.95} = \underline{2.51V}$$

$$I_L = \frac{V_L}{R_L} = 0.251A$$

$$P_L = V_L \cdot I_L = 0.63W$$

Power delivered to load is maximum when $R_L = R_{TH}$

$$\text{for } R_L = R_{TH}, V_L = \frac{V_{TH}}{R_L + R_{TH}} = \frac{V_{TH}}{2} = 1.5V$$


$$I_L \text{ for } R_L = R_{TH} : I_L = \frac{V_{TH}}{R_L} = \frac{1.5}{1.95} = 0.77A$$

$$P_{L_{MAX}} = \underline{1.154W}$$

NORTON'S EQUIVALENT :

$$R_N = R_{TH} = \underline{1.95\Omega}$$


To calculate I_N :

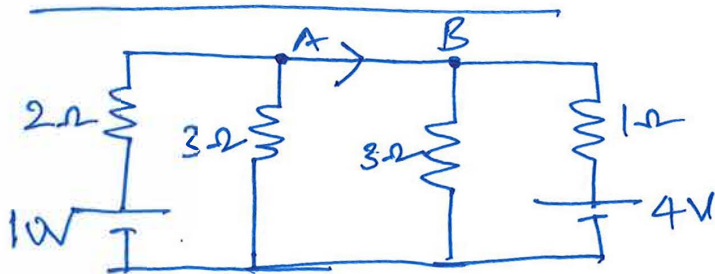

Using source transformation,

$$I_{S1} = \frac{10}{2} = 5A$$

$$I_{S2} = \frac{4}{1} = 4A$$

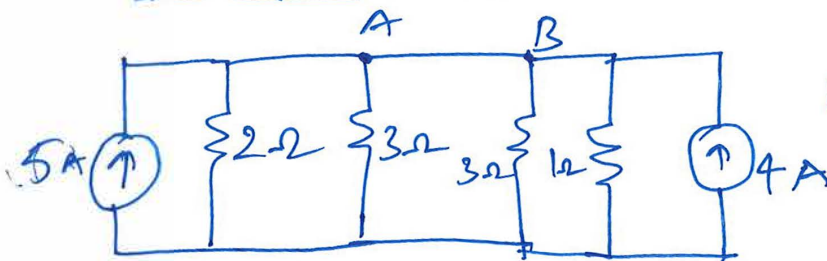


$$2 \parallel 3 = 1.2\Omega$$

$$3 \parallel 1 = 0.75\Omega$$

Using source transformation,


$$V_{s1} = 5A \times 1.2 = 6V \quad V_{s2} = 4A \times 0.75 = 3V$$

(5)

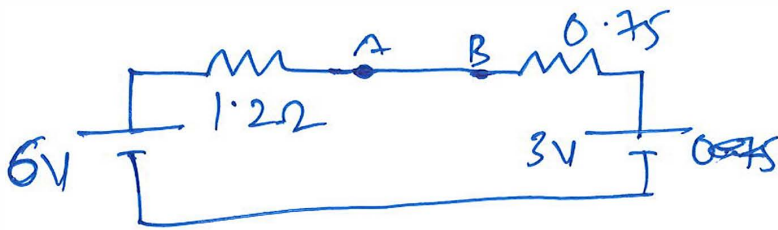

$$I_{AB} = \frac{6-3}{1.95} = 1.54A$$

$$I_N = I_{AB} = 1.54A$$

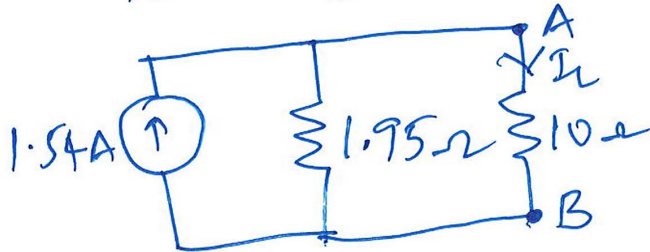


$$I_L = \frac{1.54 \times 1.95}{11.95} = 0.251A$$



$$V_L = 2.51V$$

$$P_L = V_L \cdot I_L = \underline{\underline{0.63W}}$$


Fig. 3

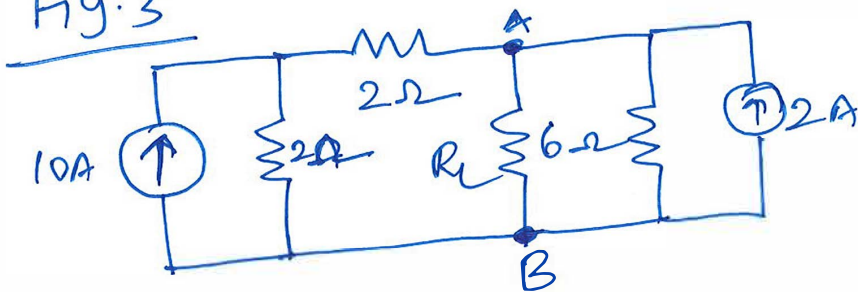

THEVENIN'S EQUIVALENT

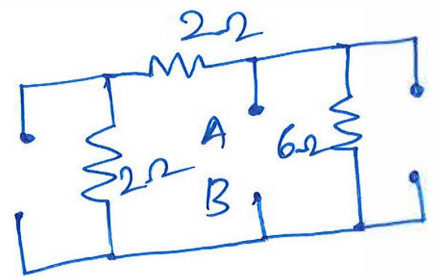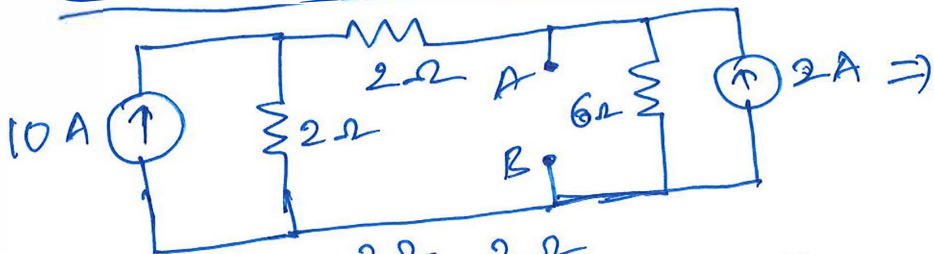

$$R_{AB} = 4 \parallel 6 = 2.4\Omega$$

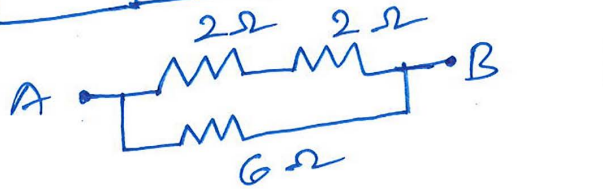


$$R_{TH} = R_{AB} = 2.4\Omega$$

To find V_{TH} :

Using Source transformation,

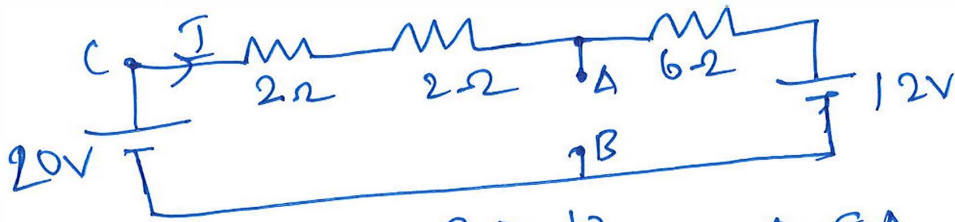$V_{S1} = 10 \times 2 = 20V$ $V_{S2} = 2 \times 6 = 12V$




$$I = \frac{20 - 12}{2 + 2 + 6} = 0.8A$$

Applying KVL for the loop ABCA,

$20 - I(2 + 2) = V_{AB} = 20 - 0.8 \times 4 = 16.8V$

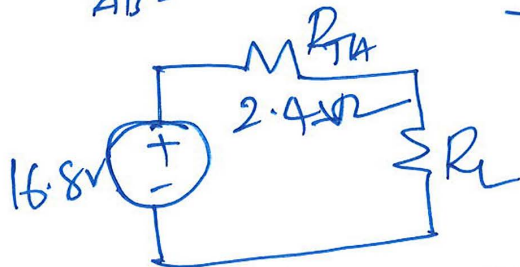$V_{AB} = 16.8V$ $V_{TH} = V_{AB} = 16.8V$



for maximum power transfer

$R_L = R_{TH} = 2.4 \Omega$


$V_L = \frac{16.8 \times 2.4}{2.4 + 2.4} = 8.4V$

$I_L = \frac{8.4}{2.4} = 3.5A$ $P_L = \frac{29.4}{2} = 14.7W$

Norton's Equivalent:


$R_N = R_{TH} = 2.4 \Omega$

To find I_N :

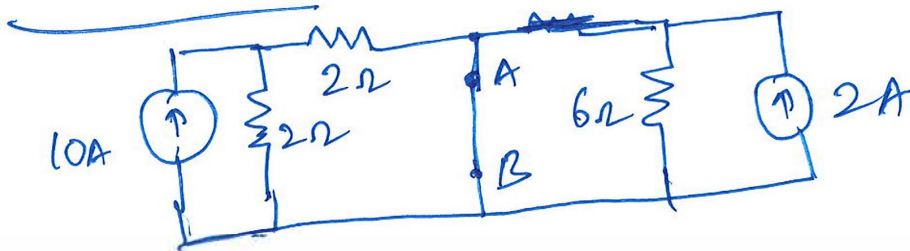


Applying Source transformation,

$$V_{S1} = 10 \times 2 = 20V$$

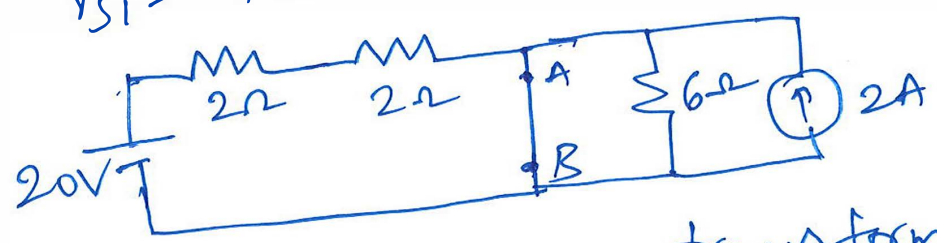


Apply source transformation,

$$I_{S1} = \frac{20}{4} = 5A$$

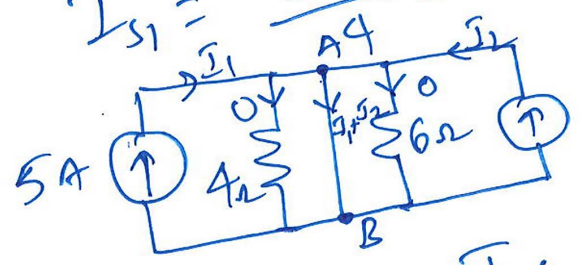

$$I_1 + I_2 = 7A$$

$$I_{AB} = 7A = I_N$$

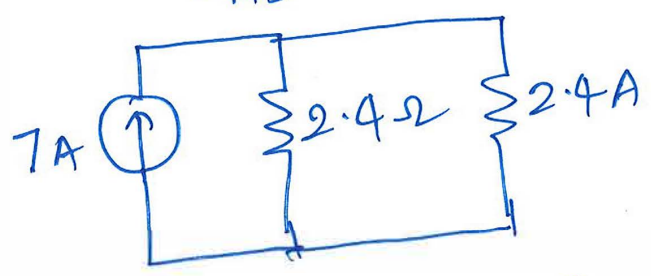


$$I_L = \frac{7 \times 2.4}{4.8} = 3.5A$$

$$V_L = I_L R_L = 8.4V$$



$$P_L = 29.4W$$

Fig. 4

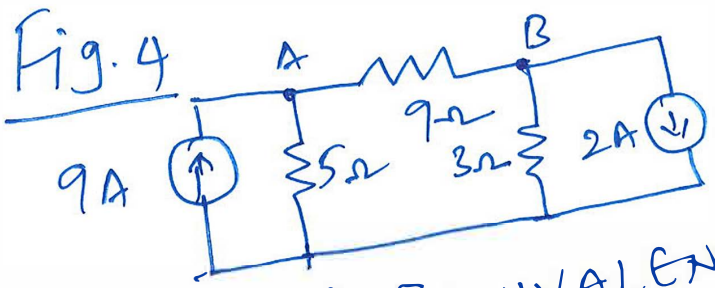

THEVENIN'S EQUIVALENT CIRCUIT :

To find R_{TH} :

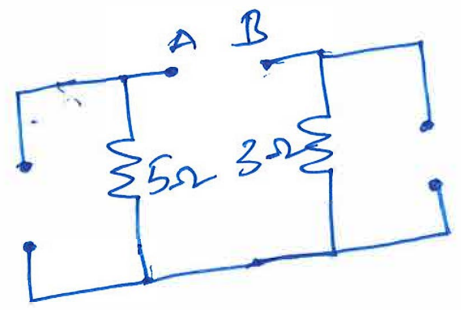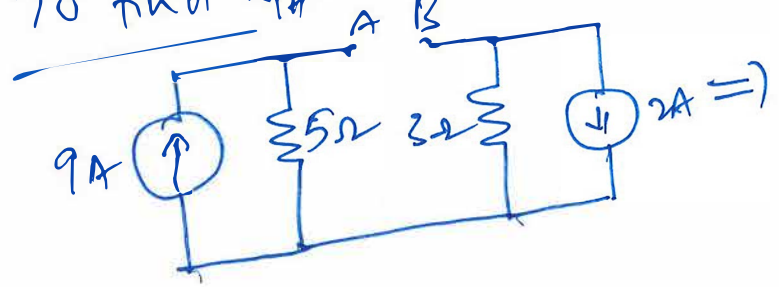


$$R_{AB} = 8\Omega$$

$$R_{TH} = R_{AB} = \underline{8\Omega}$$

(8)

To find V_{TH} :

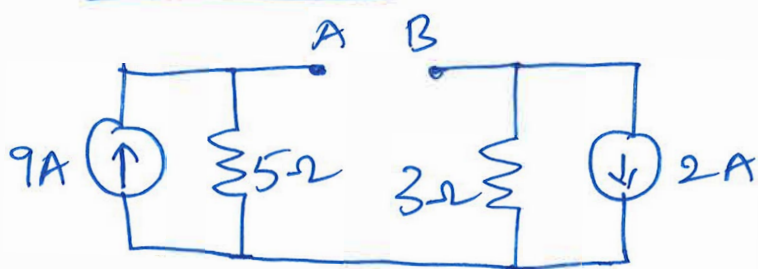

Using Source transformation

$$V_{S1} = 9 \times 5 = 45V$$

$$V_{S2} = 2 \times 3 = 6V$$



Applying KVL for the loop ABCA,

$$45 - V_{AB} + 6 = 0 \quad V_{AB} = \underline{51V}$$

$$V_{TH} = V_{AB} = \underline{51V}$$



$$V_L = \frac{51 \times 9}{9 + 8} = 27V$$

$$I_L = 27/9 = 3A$$

$$P_L = V_L I_L = 81W$$


P_L is maximum when $R_L = R_{TH}$

$$\begin{aligned} \text{Then } P_{L, \max} &= \frac{V_L \cdot R_L}{R_L + R_{TH}} \bigg|_{R_L = R_{TH}} \cdot \frac{V_L}{R_L + R_{TH}} \bigg|_{R_L = R_{TH}} \\ &= 25.5 \times \frac{25.5}{8 + 8} = \underline{\underline{81.28W}} \end{aligned}$$


NORTON'S EQUIVALENT

$$R_N = R_{TH} = 8\Omega$$

To find I_N :

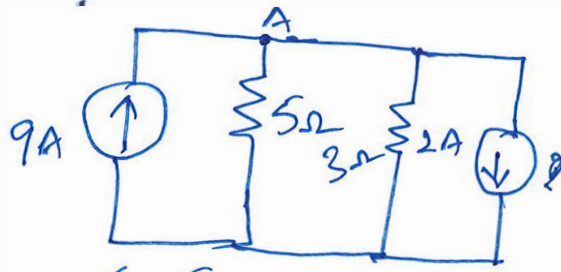


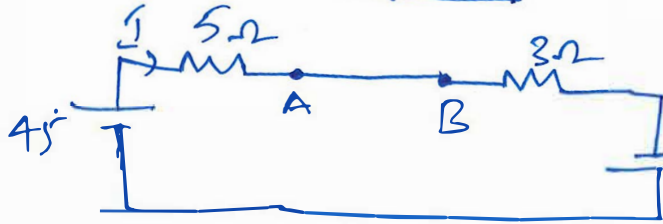Using source transformation
 $V_{S1} = 9 \times 5 = 45V$
 $V_{S2} = 2 \times 3 = 6V$



$$I = \frac{45 + 6}{8} = 6.375$$


$$I_N = 6.375$$

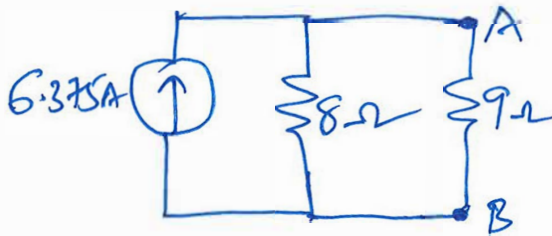

$$I_L = \frac{6.375 \times 8}{8 + 9} = 3A$$


$$V_L = I_L \cdot R_L = 3 \times 9 = \underline{27V}$$

Fig. 5

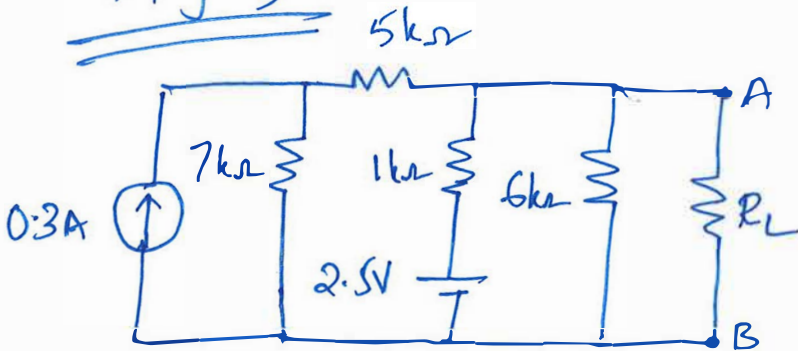



THEVENIN'S EQUIVALENT

To find R_{TH}

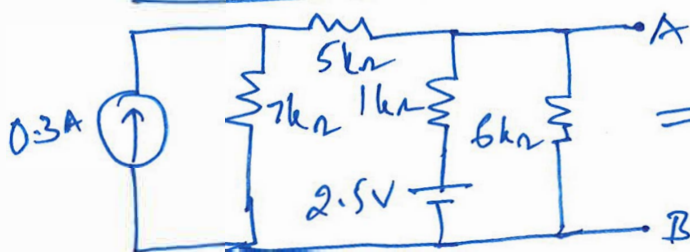
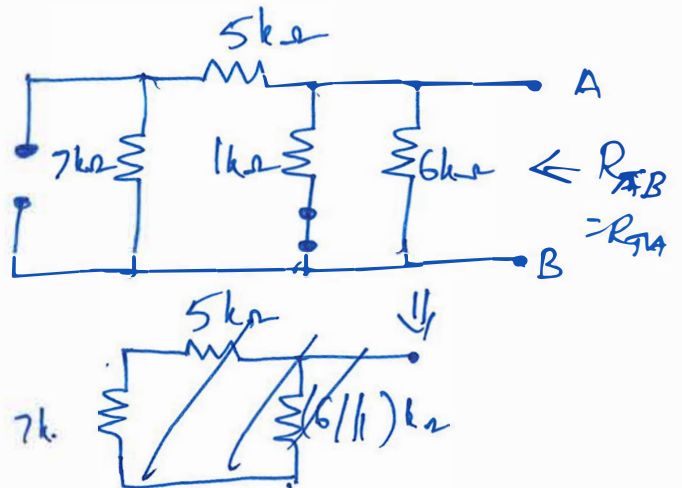
$$6k \parallel 1k = \underline{857\Omega}$$




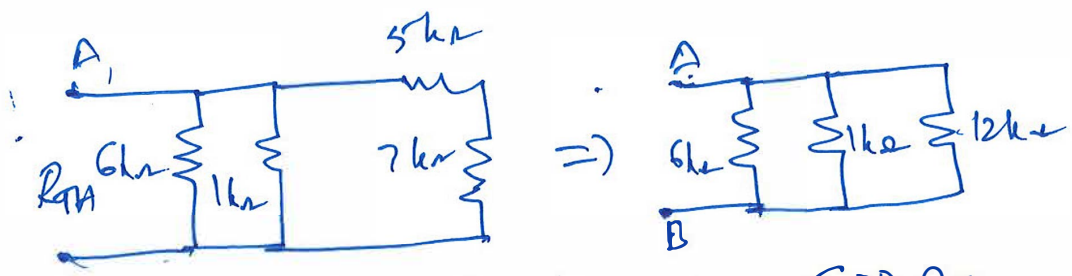

$$R_{AB} = (6k\Omega // 1k\Omega // 7k\Omega) = 800\Omega$$

$$R_{TH} = R_{AB} = 800\Omega$$


To find V_{TH}

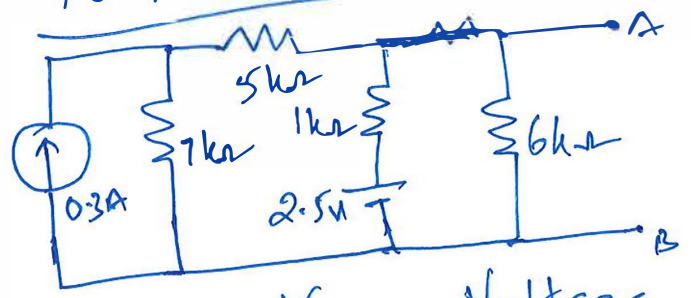

$V_{TH} = V_{AB} = V_{6k\Omega} =$ Voltage across $2.5V$ source and $1k\Omega$.


Using Source Transformation

$$V_{S1} = 0.3 \times 7k = 2100V$$

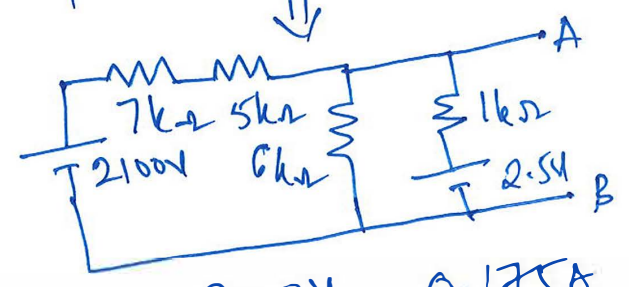


$$I_{S1} = \frac{2100V}{12k\Omega} = 0.175A$$

Using Source trans form;

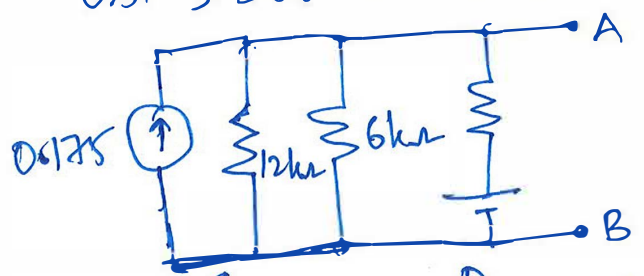

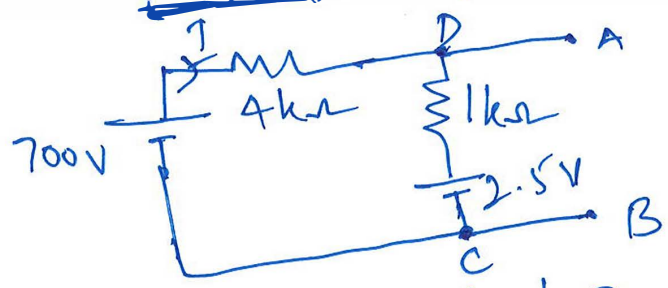$12k\Omega // 6k\Omega = 4k\Omega$
Using Source transformation,
 $V_{S1} = 0.175A \times 4k\Omega = 700V$




$$I = \frac{700 - 2.5}{5k\Omega} = 0.1395A$$

Applying KVL for loop

$$V_{TH} = V_{AB} = 142V$$

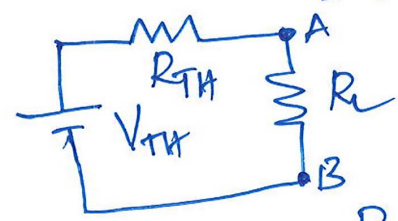ABCD, $V_{AB} = 0.1395 \times 1 \times 10^3 + 2.5 = 142V$



Maximum power is transferred when $R_L = 2R_{TH}$.

Thus, $R_L = 800\Omega$


$$I_L = \frac{V_{TH}}{R_{TH} + R_L} = \frac{142}{800 + 800} = \underline{88.75 \text{ mA}}$$

$$V_L = I_L R_L = \underline{71 \text{ V}} \quad P_L = V_L I_L = \underline{6.3 \text{ W}}$$

NORTON'S EQUIVALENT

$$R_N = R_{TH} = 800 \Omega$$

To find I_N :

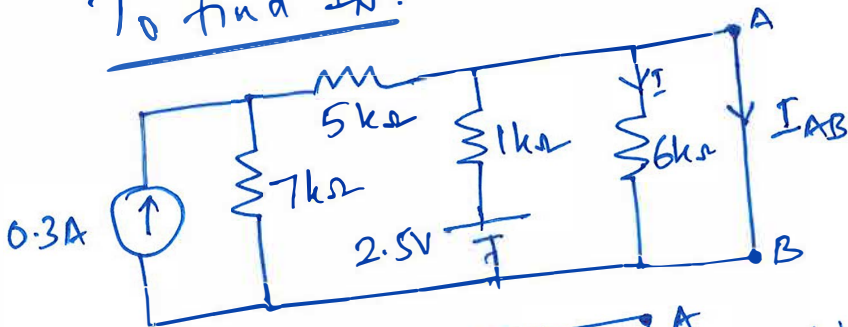

Using Source transformation



$$I_{S1} = \frac{2.5 \text{ V}}{1 \text{ k}\Omega} = 2.5 \text{ mA}$$

$$V_{S1} = 0.3 \times 7 \text{ k} = 2100 \text{ V}$$




Using Source transformation,
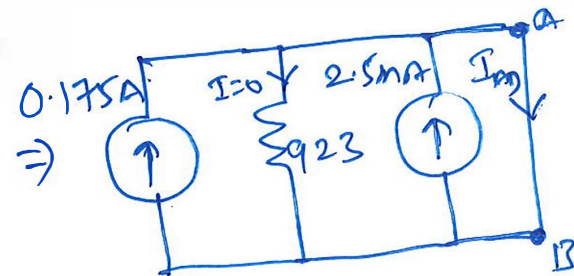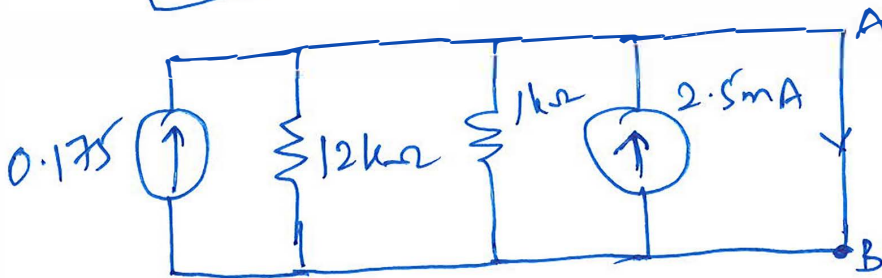
$$I_{S1} = \frac{2100}{12 \text{ k}} = 0.175 \text{ A}$$



$$I_{AB} = 0.175 \text{ A} + 2.5 \text{ mA} = \underline{177.5 \text{ mA}}$$
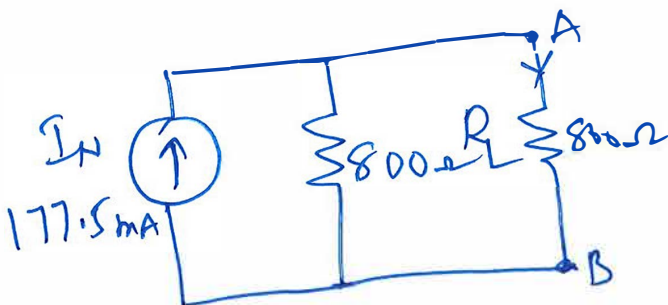
$$I_N = I_{AB} = \underline{177.5 \text{ mA}}$$




$$I_L = \frac{177.5 \text{ mA} \times 800}{800 + 800} = 88.75 \text{ mA}$$



$$V_L = 71 \text{ V}$$

$$P_L = V_L I_L = \underline{6.3 \text{ W}}$$

Fig. 6

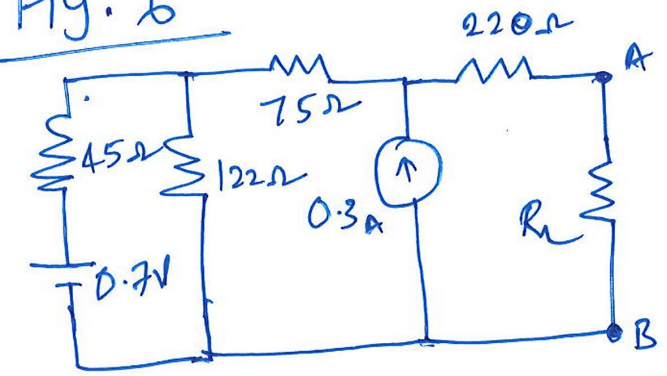


THEVENIN'S EQUIVALENT :

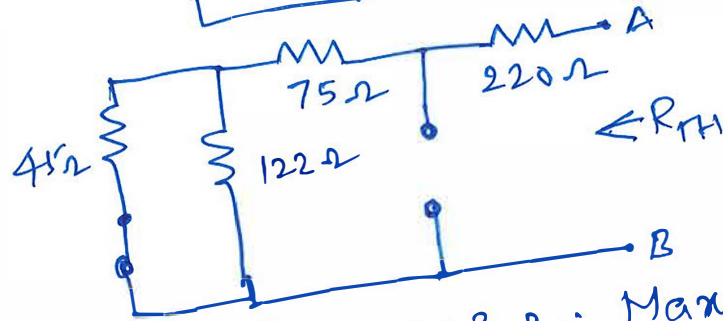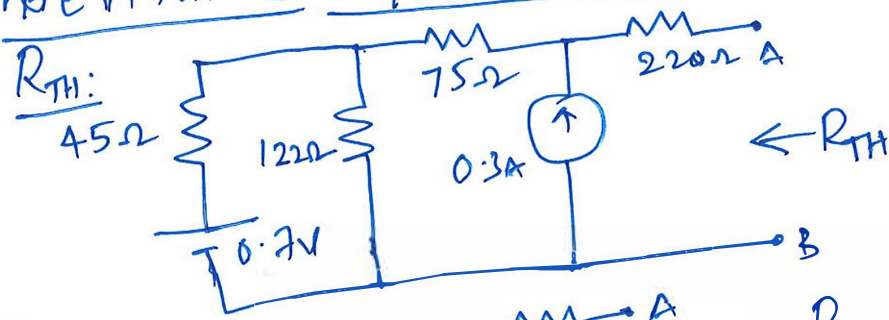


$$R_{AB} = 220 + 75 + (45 \parallel 122) = 323 \Omega$$

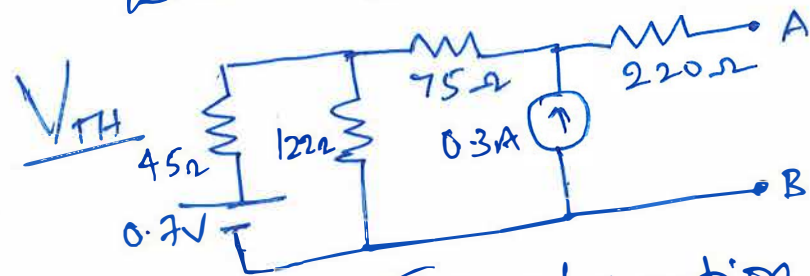$R_{TH} = R_{AB} = 323 \Omega$. Maximum power is transferred when $R_L = R_{TH}$. $R_L = 323 \Omega$




Using Source Transformation
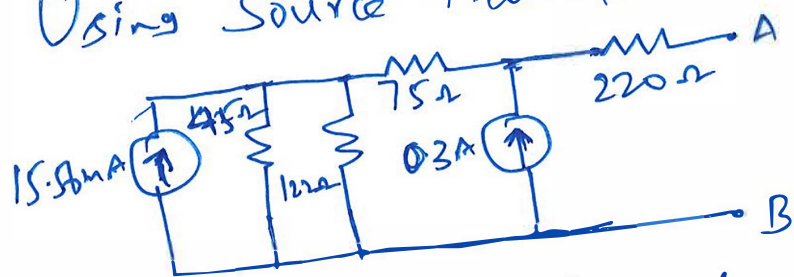
$$I_{S1} = \frac{0.7V}{45\Omega} = 15.56mA$$




$$45 \parallel 122 = 33 \Omega$$

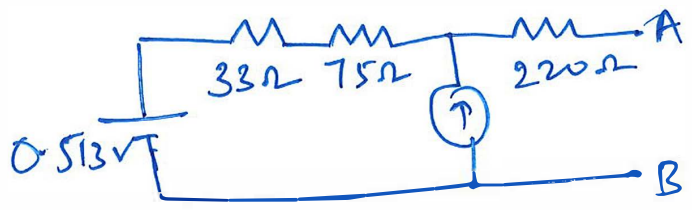Using Source transformation,
 $V_{S1} = 15.56mA \times 33 = 0.513V$



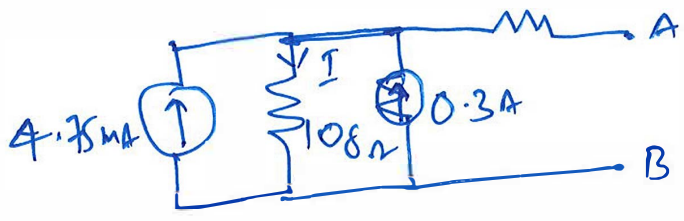
Using Source transformation,
 $I_s = \frac{0.513}{33+75} = 4.75 \text{ mA}$
 $R_s = 108 \Omega$



$I = 0.3 + 4.75 \text{ mA}$
 $= 304.75 \text{ mA}$

$V_{AB} = I \times 108 \Omega = \underline{32.913 \text{ V}}$

$V_{TH} = V_{AB} = 32.913 \text{ V}$

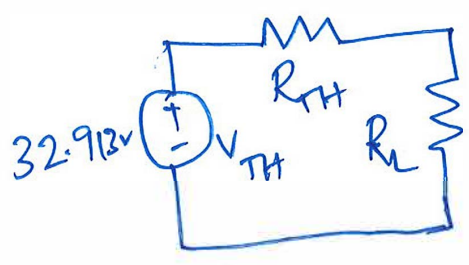

$R_{TH} = R_L = 323 \Omega$

$I_L = \frac{V_{TH}}{R_{TH} + R_L} = 50.95 \text{ mA}$


$V_L = I_L \cdot R_L = 16.4565 \text{ V}$

$P_L = V_L \cdot I_L = \underline{0.8384 \text{ W}}$

Norton's EQUIVALENT


$R_N = R_{TH} = 323 \Omega$

To find I_N :

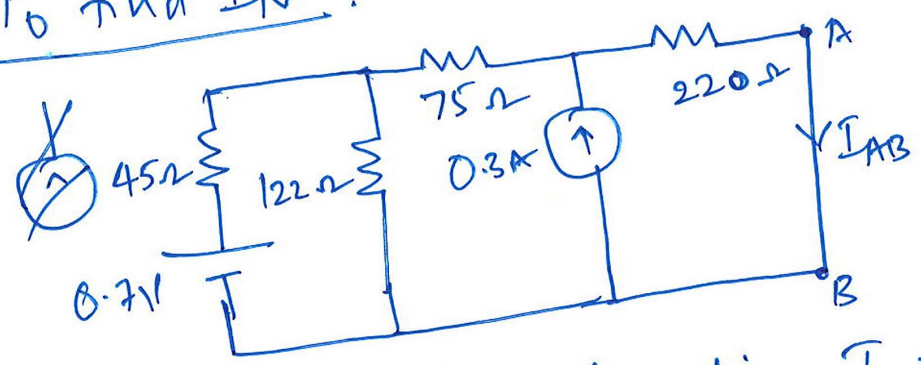

Using source transformation, $I_{s1} = \frac{0.7 \text{ V}}{45 \Omega} = 15.56 \text{ mA}$
 $45 \parallel 122 = 33 \Omega$ $R_{s1} = 33 \Omega$ $I_{s1} = 15.56 \text{ mA}$

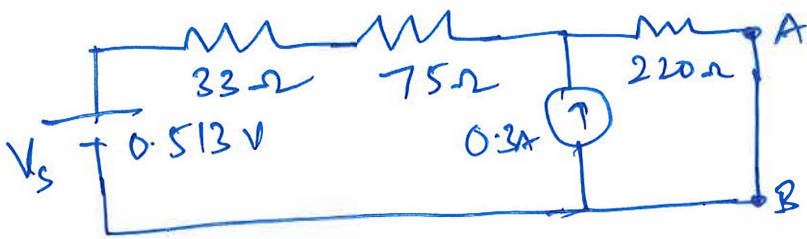Using source transformation, $V_{s1} = I_{s1} R_{s1} = \underline{0.513 \text{ V}}$




Using source trans formation, $R_s = 33 + 75 = 108 \Omega$

$$I_s = V_s / R_s = 4.75 \text{ mA}$$



$$I_2 = \frac{(0.3 + 4.75 \times 10^{-3}) \times 108}{108 + 220} = 100.3 \text{ mA}$$
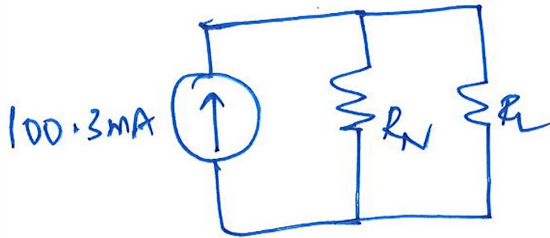
$$I_V = I_{AB} = I_2 = 100.3 \text{ mA}$$



$$R_N = R_L = 330 \Omega$$


$$I_L = 50.17 \text{ mA}$$

$$V_L = 16.56 \text{ V}$$


$$P_L = 0.83 \text{ mW}$$

(small differences are due to rounding off errors)

Fig. 7

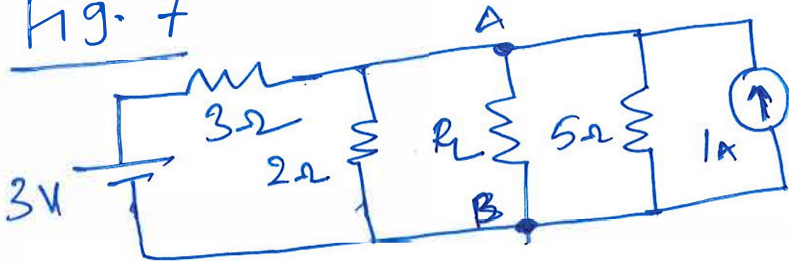

THEVENIN'S EQUIVALENT:

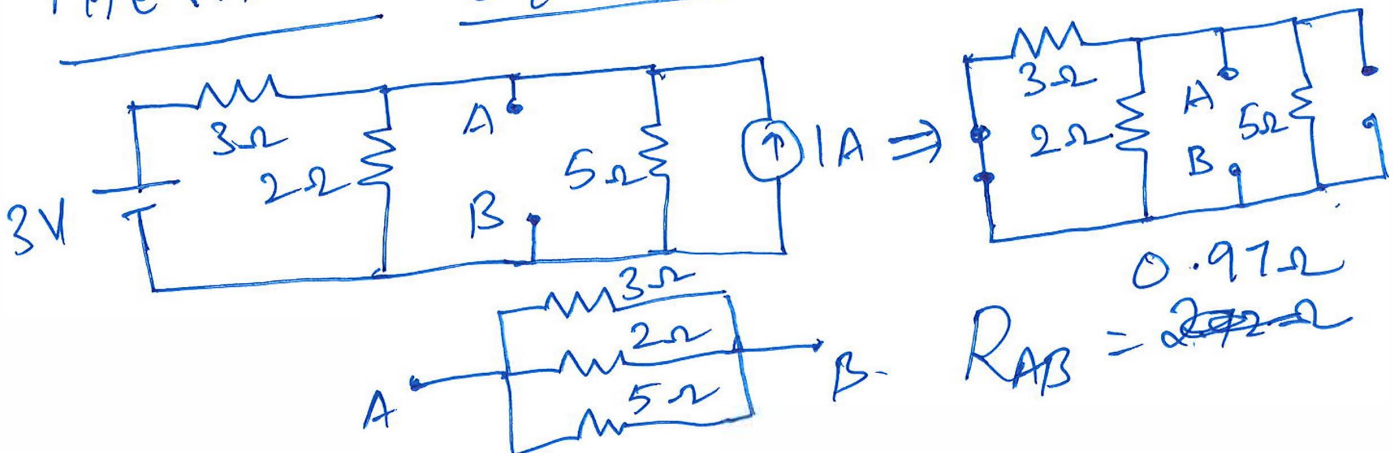


$$R_{TH} = R_{AB} = 0.97 \Omega$$

(15)

Maximum power is transferred when


$$R_L = R_{TH} \quad \text{Thus, } R_L = 0.97 \Omega$$

To find V_{TH} :

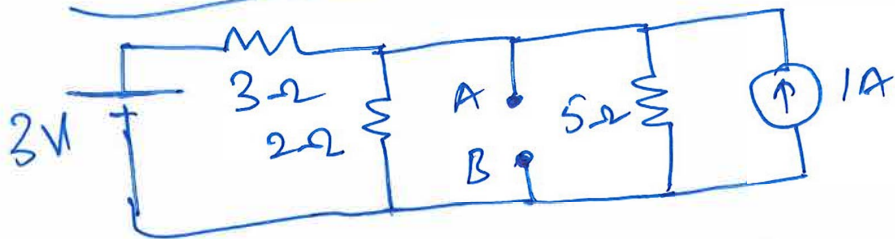

Using Source transformation,


$$I_{S1} = \frac{3V}{3\Omega} = 1A$$

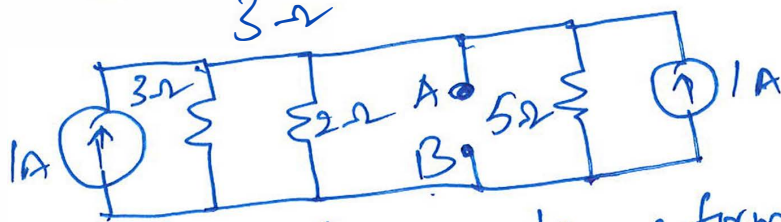

$$3 \parallel 2 = 1.2 \Omega$$

Using Source transformation, $V_{S1} = 1 \times 1.2 = 1.2V$

$$V_{S2} = 1 \times 5 = 5V$$

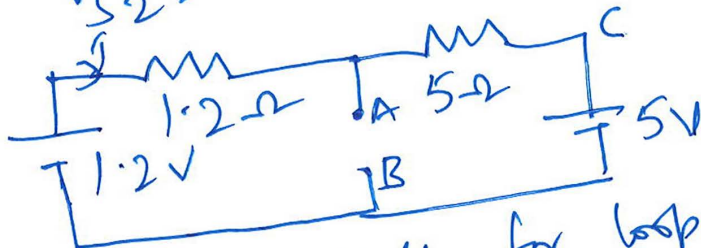


$$I = \frac{1.2 - 5}{1.2 + 5} = -0.613A$$

Applying KVL for loop ACBA,

$$V_{AB} = -5 \times 0.613 + 5 = 1.94V$$

$$V_{TH} = V_{AB} = 1.94V$$

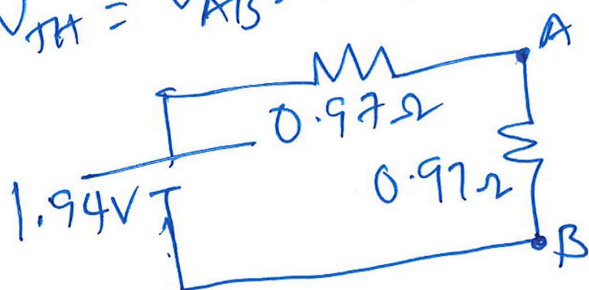

$$I_L = \frac{1.94}{2 \times 0.97} = 1A$$

$$V_L = 0.97V$$


$$P_L = V_L \cdot I_L = \underline{\underline{0.97W}}$$

Norton's Equivalent


(16)

$$R_N = R_{TH} = \cancel{1.70\Omega} \underline{0.97\Omega}$$

To find I_N :

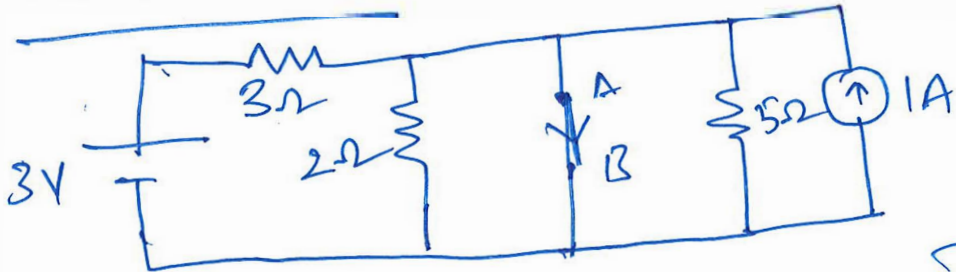


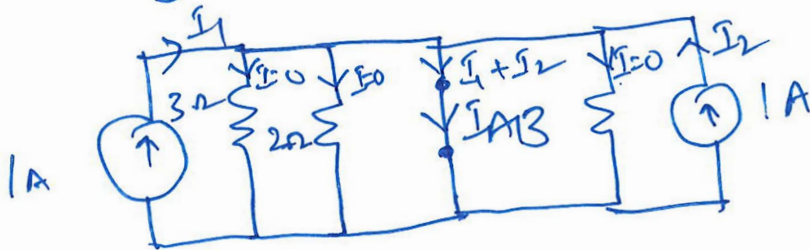Using Source transformation: $I_{S1} = \frac{3V}{2\Omega} = 1A$



$$I_{AB} = I_1 + I_2 = 2A$$

$$I_N = I_{AB} = 2A$$

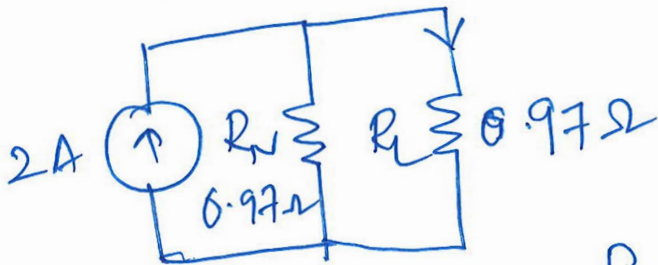

$$I_L = \frac{2 \times 0.97}{0.97 + 0.97} = 1A$$

$$V_L = I_L \cdot R_L = 0.97V$$

$$P_L = V_L I_L = \underline{0.97W}$$