

Tutorial - 10 Solutions

Inverting amplifier

①

$$V_o = -\frac{R_2}{R_1} V_{in} = \frac{15K}{1K} (0.5V) = 7.5V$$

②

$$V_o = -\frac{R_2}{R_1} V_{in} \Rightarrow R_2 = \frac{-V_o R_1}{V_{in}} = \frac{15 \times 0.5K\Omega}{0.25V}$$

$A_v = \frac{-V_o}{V_{in}}$ for inverting amplifier

Max Value of $V_o = 15V$

$$R_2 = 30K\Omega$$

③

$$R_1 = \frac{-R_2 V_{in}}{V_o} \Rightarrow \frac{7.5K \times 0.25V}{15} = 125\Omega$$

④

$$V_{in} = -\frac{V_o R_1}{R_2} \Rightarrow \frac{15 \times 1K\Omega}{10K\Omega} = 1.5V$$

Non-inverting amplifier

⑤

$$V_o = \left(1 + \frac{R_2}{R_1}\right) V_{in} = \left(1 + \frac{10K}{1K}\right) 0.5V = 5.5V$$

⑥

$$\left(\frac{V_o}{V_{in}} - 1\right) R_1 = R_2 \Rightarrow R_2 = \left(\frac{15}{0.25} - 1\right) 0.5K = 29.5K\Omega$$

⑦

$$R_1 = \frac{R_2}{\left(\frac{V_o}{V_{in}} - 1\right)} = \frac{7.5K\Omega}{\left(\frac{15}{0.25} - 1\right)} \approx 127\Omega$$

⑧

$$V_{in} = \frac{V_o}{\left(1 + \frac{R_2}{R_1}\right)} = \frac{15}{\left(1 + \frac{15K}{1K}\right)} \approx 0.94V$$

9

Summing amplifier

$$V_o = -R_f \left[\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} \right]$$

$$= -10K\Omega \left[\frac{0.5}{1K} + \frac{0.75 \sin(60\pi t)}{1.5K} + \frac{1 \sin(30\pi t)}{2K} \right]$$

$$= -10K \left[\frac{3 + 3 \sin(60\pi t) + 3 \sin(30\pi t)}{6K} \right]$$

$$V_o = - \left[\underline{5} + \underline{5} \sin(60\pi t) + \underline{5} \sin(30\pi t) \right] V$$

10

$$V_o = -\frac{R_f}{R_1} V_1 - \frac{R_f}{R_2} V_2 - \frac{R_f}{R_3} V_3$$

$$\text{Gain} = \frac{-R_f}{R_1} = \frac{-R_f}{R_2} = \frac{-R_f}{R_3} = 5$$

$$V_o = 5 \left[(0.25) + 0.75 \sin(60\pi t) + 1.2 \sin(30\pi t) \right] V$$

11

Using Superposition theorem,

output voltage of difference amplifier is

$$V_0 = \frac{R_4}{R_3 + R_4} \left[1 + \frac{R_2}{R_1} \right] V_{I2} - \frac{R_2}{R_1} V_{I1}$$

$$= \frac{9K}{12K} \left[1 + \frac{5K}{1K} \right] 0.55V - \left[\frac{5K}{1K} \right] 0.5V$$

$$= 2.475V - 2.5$$

$$V_0 = \underline{-0.025V} \quad \text{or} \quad \underline{-25mV}$$

(12)

$$V_s = 1 \sin(120\pi t)$$

$$V_o = \frac{-1}{RC} \int V_s dt$$

$$= \frac{-1}{1K \times 1\mu} \int \sin(120\pi t) dt$$

$$= \frac{-1}{10^{-3}} \left[-\frac{\cos(120\pi t)}{120\pi} \right] = \frac{1000 \cos(120\pi t)}{120\pi} \text{ V}$$

$$V_o = 2.65 \cos(120\pi t) \text{ V.}$$

(13)

$$V_o = -RC \frac{dV_s}{dt}$$

$$= -1K \times 1\mu \cdot \frac{d}{dt} [\sin(120\pi t)]$$

$$= -10^{-3} \cos(120\pi t) \times 120\pi$$

$$V_o = -0.377 \cos(120\pi t) \text{ V.}$$