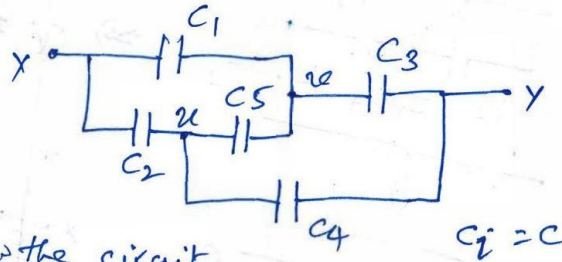


CSET102L


Tutorial Sheet - 7 (Solutions)

1)
Fig. 4




Re-draw the circuit

$$C_i = C$$

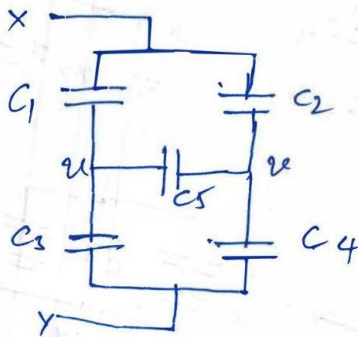


$$\therefore C_i = C,$$

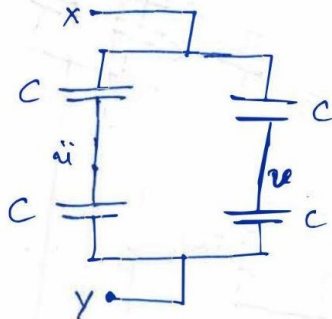Capacitors between u and v acts like a open. Thus, re-draws the circuit,





$$\Rightarrow C_{xy} = C$$

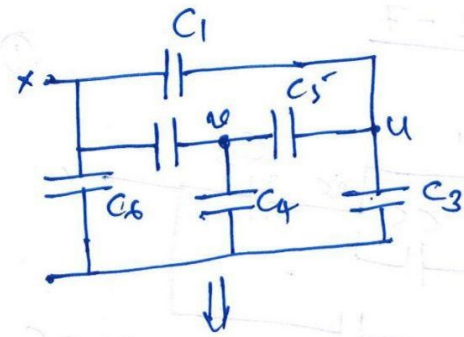Note: Fig. 6 is similar except one more capacitor is in parallel





$$\Rightarrow C_i = C$$

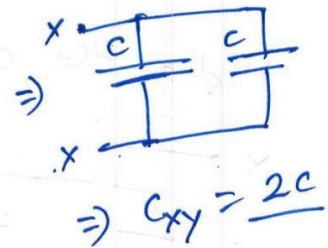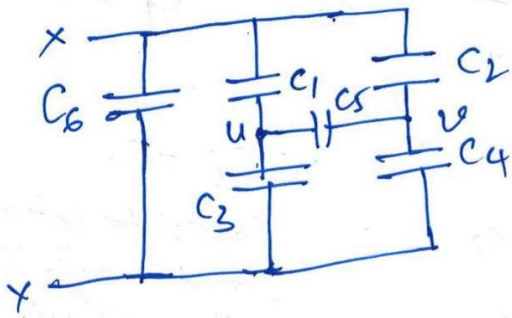


$$\Rightarrow C_{xy} = \frac{2c}{2} = c$$

Fig. 5

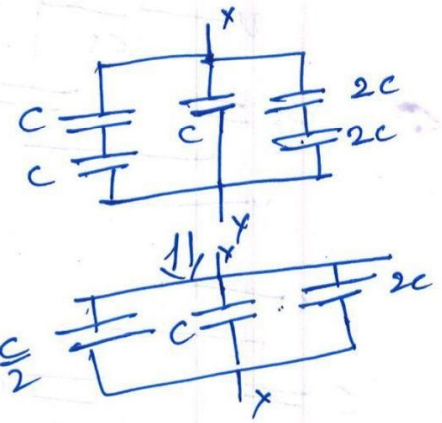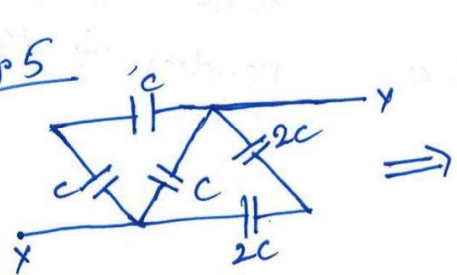

$$C_{eq} = 2.5c$$

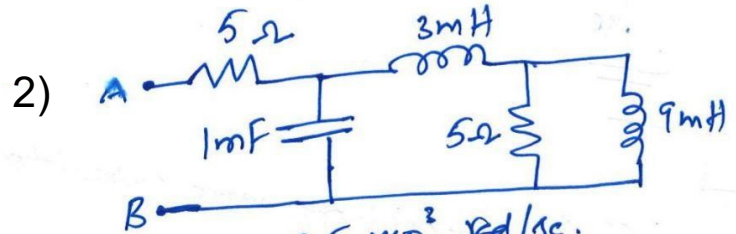

$$\omega = 2.5 \times 10^3 \text{ rad/sec.}$$

$$X_{1mF} = \frac{-j}{\omega C} = -j0.4 \Omega$$

$$X_{3mH} = j\omega L = j7.5 \Omega$$

$$X_{9mH} = j\omega L = j22.5 \Omega$$

$$5 \parallel X_{q_{MH}} = \frac{5 \times j22.5}{5 + j22.5} = \frac{112.5j(5 - j22.5)}{(5 + j22.5)(5 - j22.5)}$$

$$= \frac{562.5j + 2531.25}{(5)^2 + (22.5)^2} = 4.76 + 1.05j$$

$$(5 \parallel X_{q_{MH}}) + X_{3MH} = 4.76 + 1.05j + j7.5$$

$$= 4.76 + j8.55$$

$$X_{imp} \parallel [(5 \parallel X_{q_{MH}}) + X_{3MH}] =$$

$$= \frac{(4.76 + j8.55)(-j0.4)}{(4.76 + j8.55 - j0.4)}$$

$$= \frac{3.42 - j1.904}{(4.76 + j8.15)}$$

writing in $|z| \angle \theta$ or $r \angle \theta$ form,

$$3.42 - j1.904 = 3.91 \angle -29.1^\circ \quad \theta = \tan^{-1}(b/a)$$

$$4.76 + j8.15 = 9.438 \angle 59.71^\circ \quad r = \sqrt{a^2 + b^2}$$


$$X = \frac{3.91 \angle -29.1^\circ}{9.438 \angle 59.71^\circ} = 0.414 \angle -88.1^\circ$$

$$= -0.414j + 0.014$$

$$Z = 5 \Omega + X = 5.014 - j0.414$$

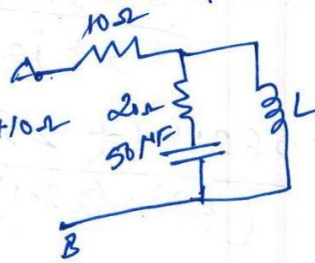3) Given $Z_{AB} = 25 + j10 \Omega$ $\omega = 4 \times 10^3 \text{ rad/sec.}$

$$Z_{AB} = \left[j\omega L \parallel \left(20 - \frac{j}{\omega C} \right) \right] + 10 \Omega$$



$$25 + j10 = 10 + j\omega L$$

$$20 - \frac{j}{\omega C} = 20 - j5$$

$$j\omega L \parallel (20 - j5) = \frac{j\omega L (20 - j5)}{(20 - j5 + j\omega L)}$$

$$25 + j10 - 10 = \frac{j20\omega L + 5\omega L}{(20 + j(\omega L - 5))}$$

$$(15 + j10) [20 + j(\omega L - 5)] = 5\omega L + j20\omega L$$

Equating real parts

$$300 - 10\omega L + 50 = 5\omega L \Rightarrow L = \underline{5.83 \text{ mH}}$$


Equating imaginary parts,

$$200j - 75j + j15\omega L = 20\omega L$$

$$125 = 5\omega L \Rightarrow L = \underline{6.25 \text{ mH}}$$

So two inductance values are possible.


4)

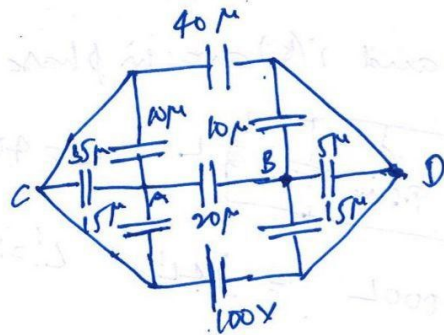

$$10\mu \parallel 35\mu \parallel 15\mu = 60\mu F$$

$$5\mu \parallel 15\mu \parallel 10\mu = 30\mu F$$

re-drawing circuit,

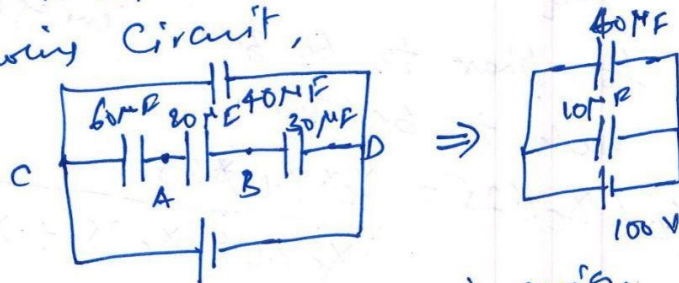

As $60\mu F, 20\mu F, 30\mu F$ are in series,

$$C_{eq} = \left[\frac{1}{60} + \frac{1}{20} + \frac{1}{30} \right]^{-1} = 10\mu F$$

$$10\mu F \parallel 40\mu F = 30\mu F$$

$$Q = C_{eq} V = 50 \times 10^{-6} \times 100 = 5000\mu C$$

Charge in $10\mu F$ capacitance is $100 \times 10\mu F = 1000\mu C$

So charge on $20\mu F$ capacitance is 200


So voltage across $20\mu F$ capacitance is

$$V = \frac{Q}{C} = 50V$$

So the energy stored in the capacitor is given by $\frac{1}{2} CV^2 = 0.025 W$


Filters

1)

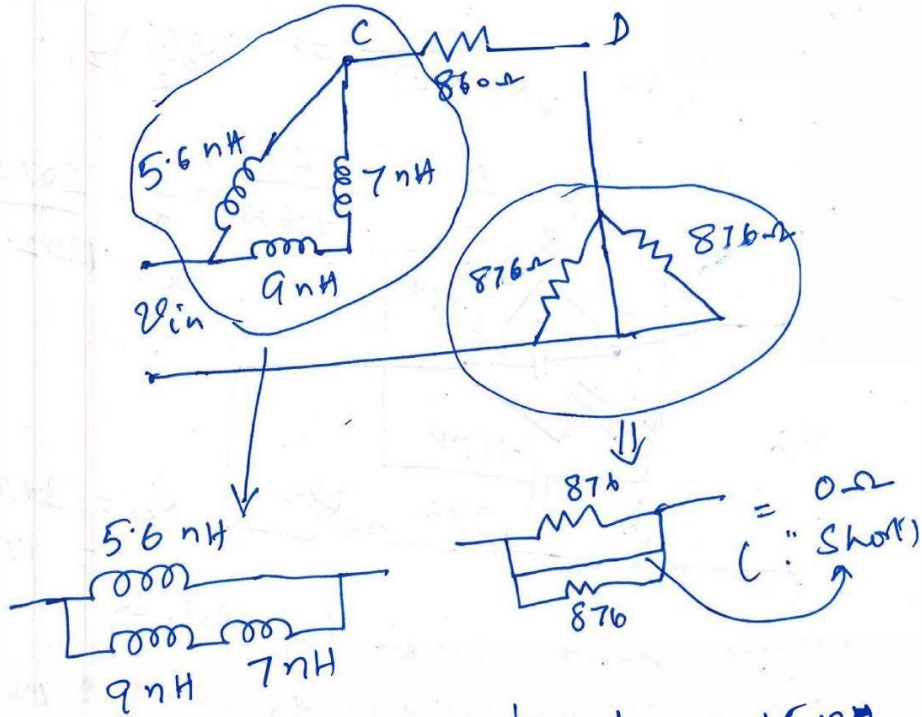

$$\frac{1}{L_{eq}} = \frac{1}{(9n+7n)} + \frac{1}{(5.6n)} \Rightarrow L_{eq} = \underline{4.15nH}$$

Re-drawing the circuit

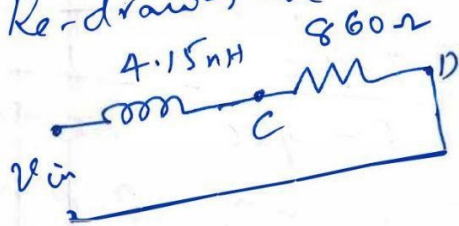

$$H(\omega) = \frac{V_R}{V_R + V_L}$$

$$= \frac{R}{R + j\omega L}$$

$$|H(\omega)| = \frac{R}{\sqrt{R^2 + \omega^2 L^2}} = \frac{1}{(1 + \omega^2 \cdot 2.38 \times 10^{-22})^{1/2}}$$

at $\omega = 0$, $|H(\omega)| = 1$
 at $\omega \rightarrow \infty$, $|H(\omega)| = 0$ } Thus a lowpass filter


when $|H(\omega)| = \frac{1}{\sqrt{2}}$

$$\frac{1}{\sqrt{2}} = \frac{R}{\sqrt{R^2 + (\omega L)^2}} \Rightarrow \omega \left(\frac{L}{R}\right) = 1$$

$$\omega_c = \frac{R}{L} = \frac{860}{4.6 \times 10^{-9}} \frac{1}{s} = \underline{207.3 \text{ rad/sec}}$$

$$f_c = 32.98 \text{ GHz}$$

2)

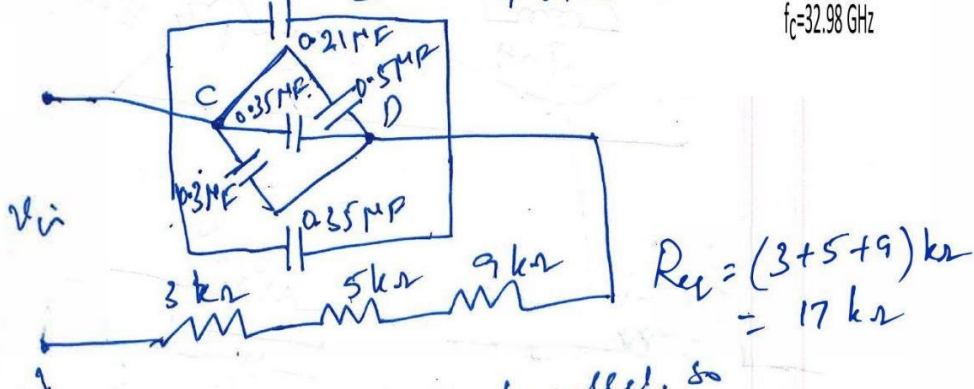


All the capacitors are in parallel. so

$$C_{eq} = (0.21 + 0.5 + 0.35 + 0.35) \text{ MF}$$

$$= 1.71 \text{ MF}$$

Re-drawing the circuit

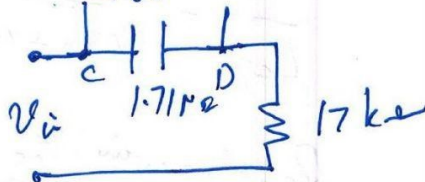

$$H(\omega) = \frac{V_c}{V_R + V_c} = \frac{-j/\omega C}{R - j/\omega C} = \frac{1}{1 + j\omega RC}$$

$$|H(\omega)| = \frac{1}{\sqrt{1 + (\omega RC)^2}} \quad \text{when } \omega = 0 \Rightarrow |H(\omega)| = 1$$


Low pass filter $\Leftrightarrow \begin{cases} |H(\omega)| = 1 \\ |H(\omega)| = 0 \text{ for } \omega = \infty \end{cases}$

$$|H(\omega)| = \frac{1}{\sqrt{2}} \Rightarrow \omega_c RC = 1 \Rightarrow f_c = \frac{1}{2\pi RC}$$

$$f_c = \underline{5.47 \text{ Hz}}$$

$$|H(\omega)| = \frac{1}{\sqrt{1 + (0.029)^2 \omega^2}}$$


3)

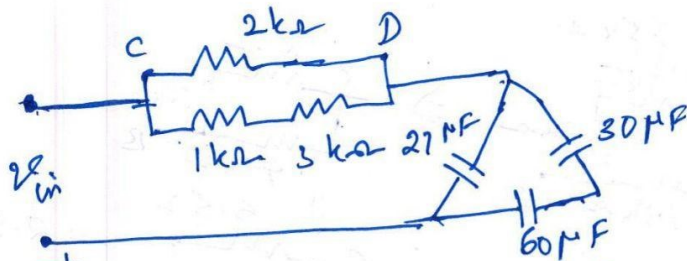

$$R_{eq} = \frac{1}{2k} + \frac{1}{(1k+3k)} \Rightarrow R_{eq} = \frac{4}{3} k\Omega$$

$$C_{eq} = 27nF + \frac{1}{\left(\frac{1}{60n} + \frac{1}{30n}\right)} = (27+20)nF = 47nF$$

Equivalent circuit: 47nF

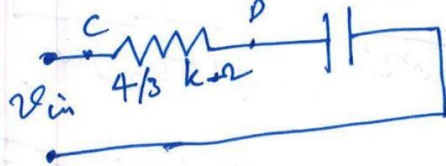


$$H(\omega) = \frac{V_R}{V_R + V_C}$$

$$|H(\omega)| = \frac{R}{\sqrt{R^2 + \frac{1}{\omega^2 C^2}}} = \frac{1}{\sqrt{1 + \frac{1}{(\omega RC)^2}}} = \frac{\omega RC}{\sqrt{1 + (\omega RC)^2}}$$

$$\left. \begin{array}{l} \omega \rightarrow 0 \Rightarrow H(\omega) \rightarrow 0 \\ \omega \rightarrow \infty \Rightarrow H(\omega) \rightarrow 1 \end{array} \right\} \rightarrow \text{High pass filter}$$


$$|H(\omega)| = \frac{0.063\omega}{\sqrt{1 + 4 \times 10^3 \omega^2}} \quad f_c = \frac{1}{2\pi RC} = 2.54 \text{ kHz}$$

4)

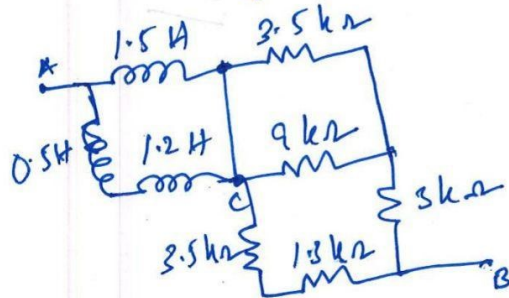


$$L_{eq} = \frac{1}{1.5} + \frac{1}{(1.2+0.5)}$$

$$\Rightarrow L_{eq} = 0.8H$$

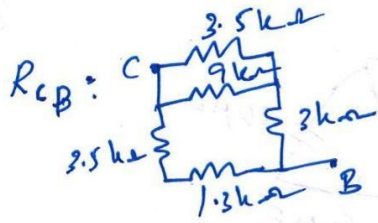

\Rightarrow

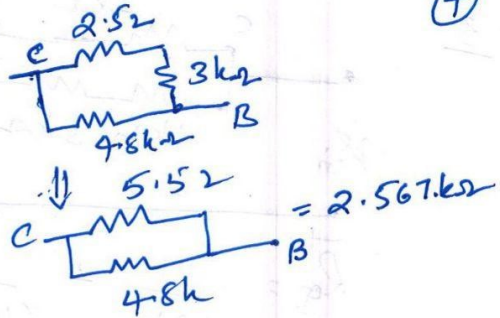

$$H(\omega) = \frac{V_R}{V_L + V_C} = \frac{R}{j\omega L + R}$$

$$|H(\omega)| = \frac{R}{\sqrt{R^2 + \omega^2 L^2}} = \frac{1}{\sqrt{1 + \left(\frac{L}{R}\right)^2 \omega^2}}$$

$$= \frac{1}{\sqrt{1 + 0.097 \omega^2 \times 10^{-6}}}$$

$\omega \rightarrow 0 \quad |H(\omega)| \rightarrow 1$
 $\omega \rightarrow \infty \quad |H(\omega)| \rightarrow 0$
} \Rightarrow low pass filter

$f_c: |H(\omega)| = \frac{1}{\sqrt{2}} \Rightarrow \frac{1}{2} = \frac{1}{1 + 0.097 \omega^2 \times 10^{-6}}$

$$\omega_c = \frac{1}{\sqrt{0.97}} \quad f_c = \frac{1}{2\pi \times \sqrt{0.97} \times 10^{-6}} = \underline{\underline{510 \text{ Hz}}}$$