

Department of ECE, Bennett University

CSET102: Introduction to Electrical and Electronics Engineering

Tutorial Sheet-3

Topics Covered: Mesh and Nodal Analysis

1. Consider the circuits shown in fig. 1 through fig. 5. Using Nodal analysis, solve for currents and voltages across all the resistances in a given circuit.

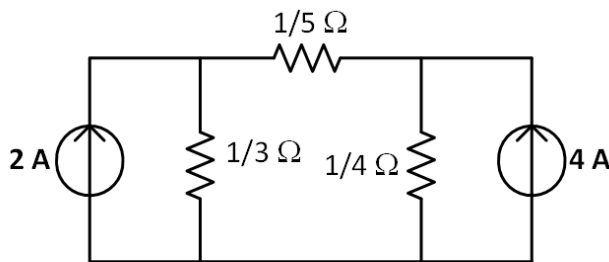


Fig. 1

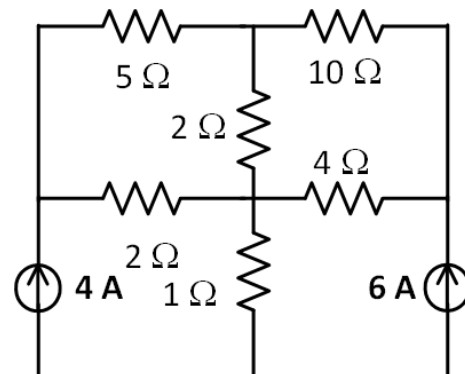


Fig. 2

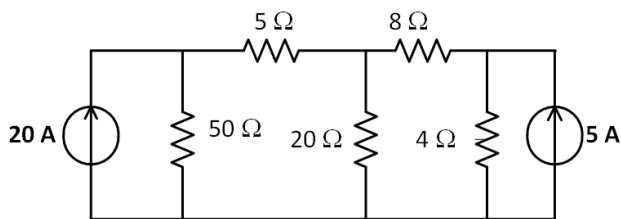


Fig. 3

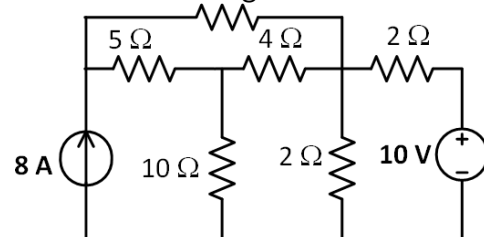


Fig. 4

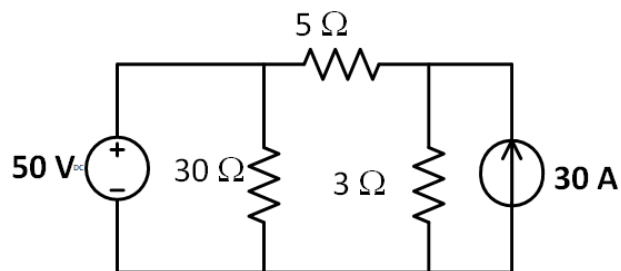


Fig. 5

2. Consider the circuits shown in fig. 6 through fig. 11. Using Mesh analysis, solve for currents and voltages across all the resistances in a given circuit.

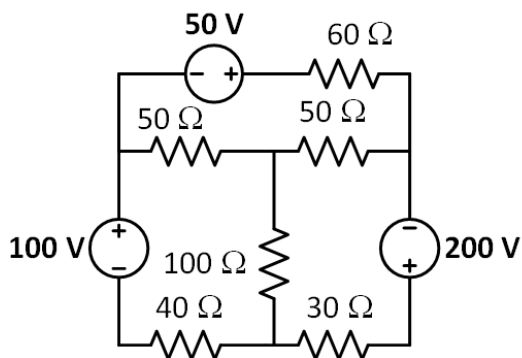


Fig. 6

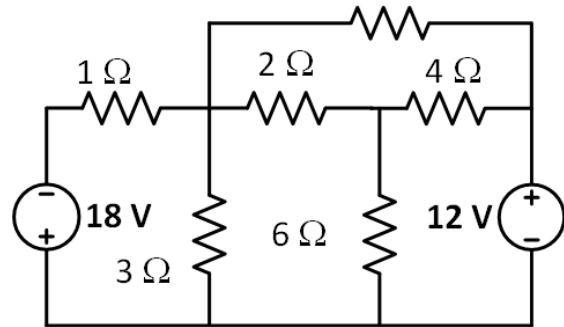


Fig. 7

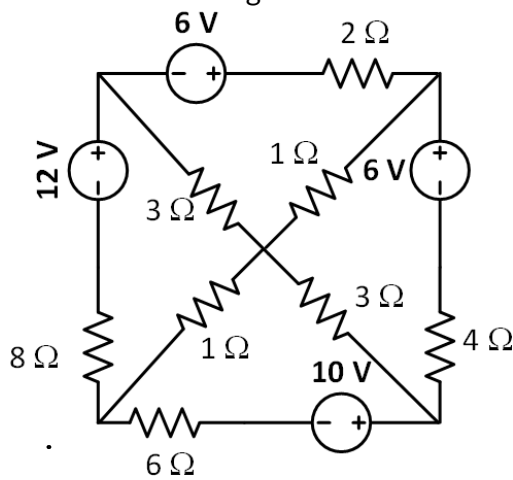


Fig. 8

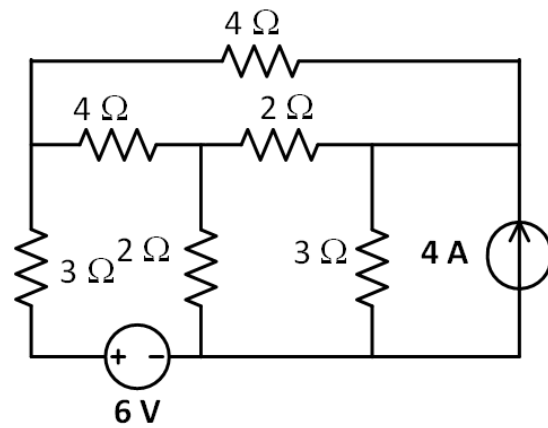


Fig. 9

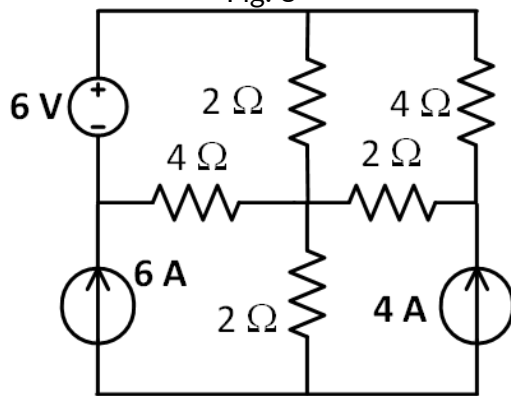


Fig. 10

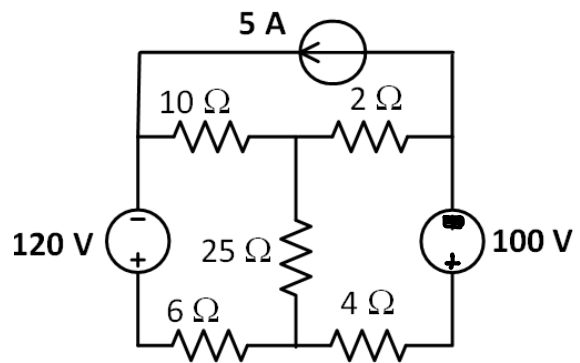


Fig. 11

----- END OF QUESTIONS -----

Answers:

1. Fig. 1: $V_1 = 0.8085$ V, $V_2 = 0.8936$ V; $I_{0.2\Omega} = -0.4255$ A; $I_{0.33\Omega} = 2.4255$ A, $I_{0.25\Omega} = 3.5744$ A

Fig. 2: $V_1 = 16.8571$ V, $V_2 = 28.2857$ V, $V_3 = 14$ V, $V_4 = 10$ V; $I_{2\Omega} = 3.43$ A, $I_{5\Omega} = 0.57$ A, $I_{4\Omega} = 4.57$ A, $I_{10\Omega} = 1.43$ A, $I_{2\Omega} = 2$ A, $I_{1\Omega} = 10$ A

Fig. 3: $V_1 = 210$ V, $V_2 = 131$ V, $V_3 = 57$ V; $I_{5\Omega} = 15.8$ A, $I_{50\Omega} = 4.2$ A, $I_{8\Omega} = 9.25$ A, $I_{20\Omega} = 6.55$ A, $I_{4\Omega} = 14.25$ A

Fig. 4: $V_1 = 34.43$ V, $V_2 = 11.24$ V, $V_3 = 17.63$ V; $I_{5\Omega} = 3.36$ A, $I_{10\Omega} = 1.763$ A, $I_{4\Omega} = 1.5975$ A, $I_{5\Omega} = 4.838$ A, $I_{2\Omega} = 5.62$ A

Fig. 5: $V_1 = 50$ V, $V_2 = 75$ V; $I_{5\Omega} = 5$ A, $I_{30\Omega} = 1.67$ A, $I_{3\Omega} = 25$ A, $I_{source} = 3.33$ A

2. Fig. 6: $I_1 = 2.873$ A, $I_2 = 3.333$ A, $I_3 = 2.252$ A

| | | | | | | |
|-------|-------------|--------------|-------------|-------------|-------------|-------------|
| | 40 Ω | 100 Ω | 60 Ω | 50 Ω | 50 Ω | 30 Ω |
| I (A) | 2.873 | -0.46 | 2.252 | -1.081 | -0.621 | 3.333 |
| V (V) | 114.92 | -46 | 135.12 | -54.05 | -31.05 | 100 |

Fig. 7: $I_1 = -9.182$ A, $I_2 = -6.243$ A, $I_3 = -5.987$ A, $I_4 = -2.602$ A

| | | | | | | |
|-------|------------|------------|------------|------------|------------|------------|
| | 1 Ω | 3 Ω | 6 Ω | 8 Ω | 2 Ω | 4 Ω |
| I (A) | -9.182 | -2.939 | -0.256 | -2.602 | 3.641 | 3.385 |
| V (V) | -9.182 | -8.817 | -1.536 | -20.816 | 9.884 | 13.54 |

Fig. 8: $I_1 = -1.1754$ A, $I_2 = 1.2687$ A, $I_3 = 1.4664$ A, $I_4 = -1.0075$ A

| | | | | | | | | |
|-------|------------|------------|------------|------------|------------|------------|------------|------------|
| | 6 Ω | 8 Ω | 2 Ω | 4 Ω | 1 Ω | 1 Ω | 3 Ω | 3 Ω |
| I (A) | -1.1754 | 1.2687 | 1.4664 | -1.0075 | 2.4441 | 2.4739 | 0.1977 | 0.1679 |
| V (V) | 7.0524 | 10.1496 | 2.9328 | -4.03 | 2.4441 | 2.4739 | 0.5931 | 0.5037 |

Fig. 9: $I_1 = -1.7561$ A, $I_2 = 0.1469$ A, $I_3 = -0.2927$ A

| | | | | | | |
|-------|------------|------------|------------|------------|------------|------------|
| | 3 Ω | 2 Ω | 2 Ω | 3 Ω | 4 Ω | 4 Ω |
| I (A) | -1.7561 | -1.9023 | -1.4634 | .1463 | 0.439 | -0.2927 |
| V (V) | -5.2683 | -3.8046 | -2.9268 | 0.4369 | 1.756 | -1.1708 |

Fig. 10: $I_1 = 5.09$ A, $I_2 = 0.273$ A, $I_3 = -4$ A, $I_4 = 6$ A

| | | | | | |
|-------|------------|------------|------------|------------|------------|
| | 2 Ω | 4 Ω | 4 Ω | 2 Ω | 2 Ω |
| I (A) | 5.09 | -0.91 | 0.273 | 4.273 | 10 |
| V (V) | 10.18 | -3.64 | 1.092 | 8.546 | 20 |

Fig. 11: $I_1 = -4.675$ A, $I_2 = -0.867$ A, $I_3 = -5$ A

| | | | | | |
|-------|-------------|------------|------------|-------------|------------|
| | 10 Ω | 2 Ω | 4 Ω | 25 Ω | 6 Ω |
| I (A) | -0.325 | -4.133 | -0.867 | -3.808 | -4.675 |
| V (V) | -3.25 | -8.266 | -3.468 | -95.2 | -28.05 |