

Department of ECE, Bennett University

CSET102: Introduction to Electrical and Electronics Engineering

Tutorial Sheet-7

Topics Covered: Capacitance, Inductance, Impedance

1. Find the equivalent capacitance of the networks shown in fig. 1 through fig. 6.

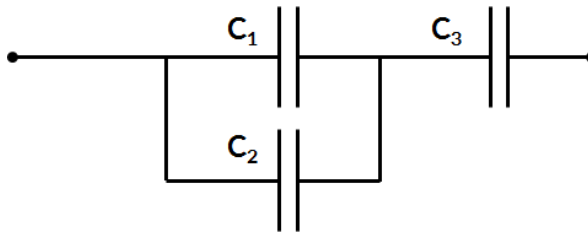


Fig. 1

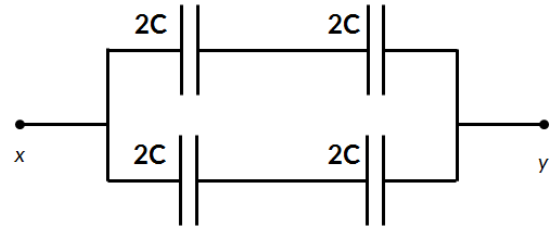


Fig. 2

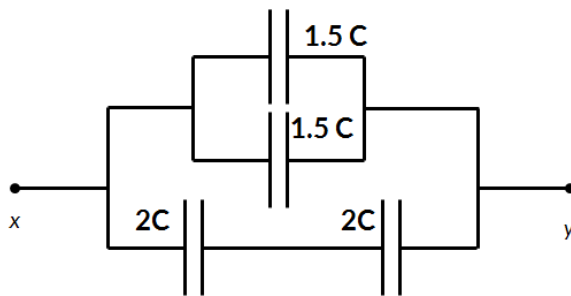


Fig. 3

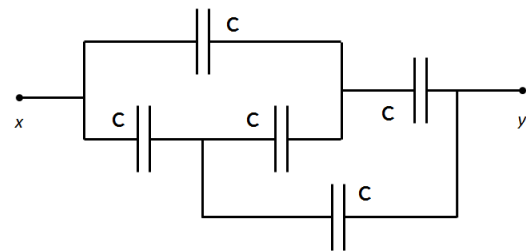


Fig. 4

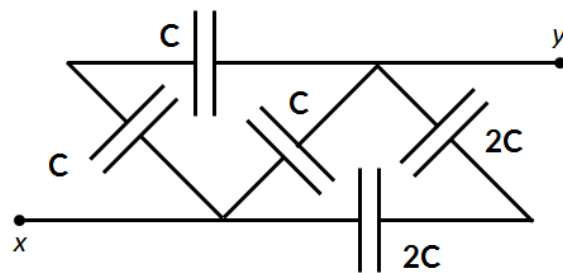


Fig. 5

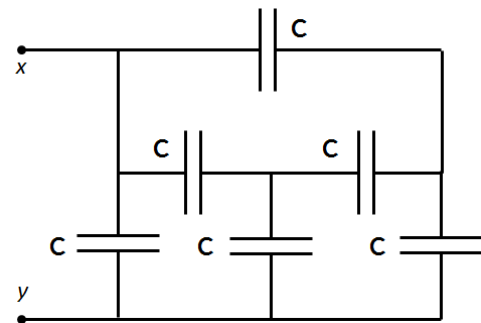


Fig. 6

2. Find the equivalent impedance (impedance between points A and B for the circuit shown in Fig. 7. Given that $\omega = 2.5 \times 10^3$ rad/sec.

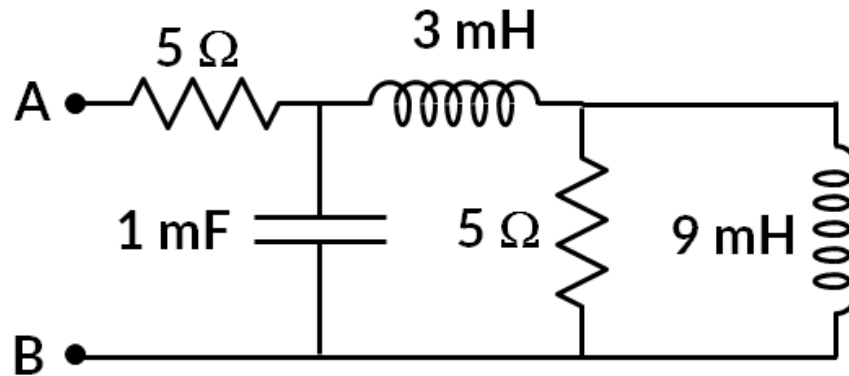


Fig. 7

3. For the circuit shown in Fig. 8, for $\omega = 4000$ rad/sec, the impedance across A and B is $(25 + j10) \Omega$. What is the value of inductor?

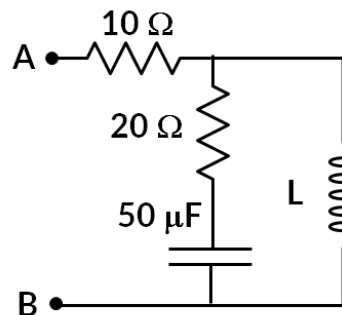


Fig. 8

4. In the circuit shown in Fig. 9, find the charge and energy stored by the $20 \mu\text{F}$ capacitor.

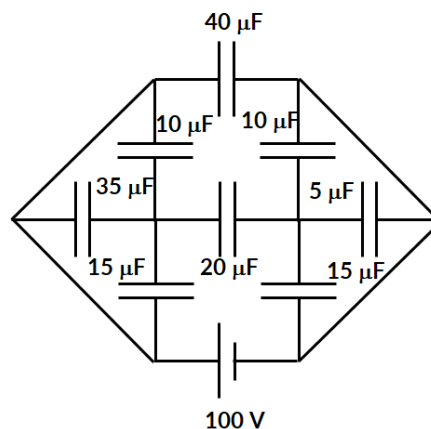


Fig. 9

Topics Covered: Filter Circuits

- For the circuit shown in Fig. 1, identify the filter type, find the transfer function and cut-off frequency of the filter. The output of the filter is taken between nodes C and D.

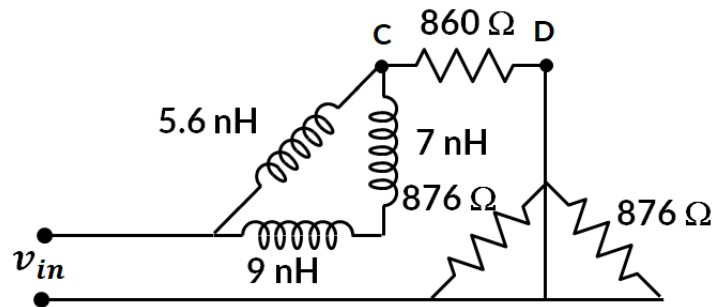


Fig. 1

- For the circuit shown in Fig. 2, identify the filter type, find the transfer function and cut-off frequency of the filter. The output of the filter is taken between nodes C and D.

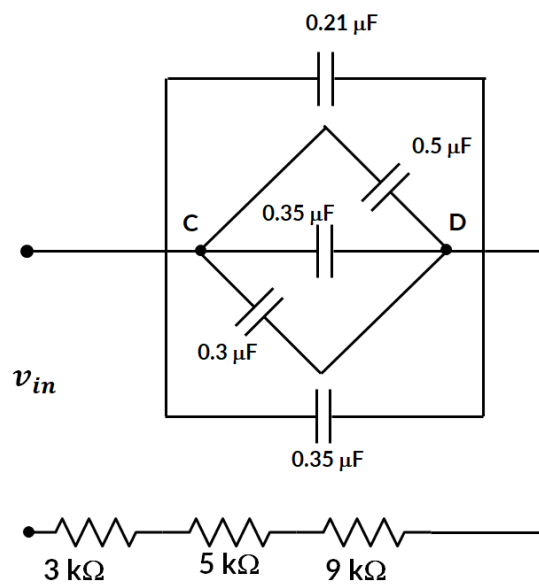


Fig. 2

3. For the circuit shown in Fig. 3, identify the filter type, find the transfer function and cut-off frequency of the filter. The output of the filter is taken between nodes C and D.

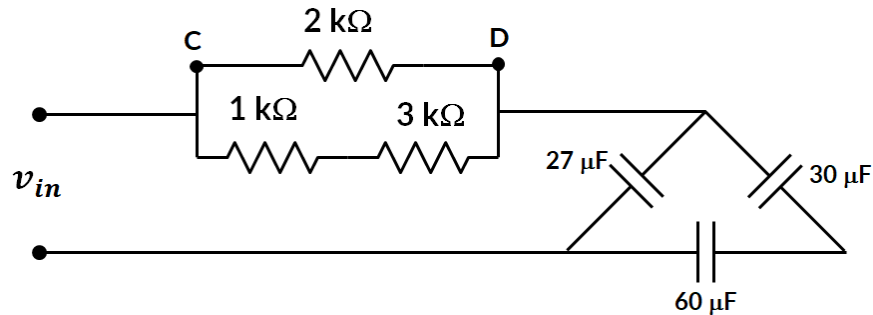


Fig. 3

4. For the circuit shown in Fig. 4, identify the filter type, find the transfer function and cut-off frequency of the filter. Input and output to the filter are between A and B; B and C respectively.

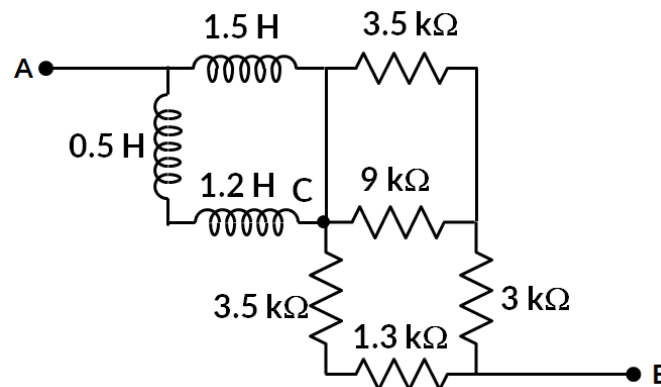


Fig. 4

----- END OF QUESTIONS -----

Answers:

1)

Fig. 1	$C_{eq} = \frac{(C_1 + C_2)C_3}{C_1 + C_2 + C_3}$
Fig. 2	2C
Fig. 3	4C
Fig. 4	C
Fig. 5	2.5 C
Fig. 6	2C

 2) $(5.014 - j0.414)\Omega$

3) 6.25 mH

 4) 1000 μ C, 0.025 W

Filters:

$$1) f_c = 32.98 \text{ GHz}, |H(\omega)| = \frac{1}{\sqrt{1+2.38 \times 10^{-23} \omega^2}}$$

$$2) f_c = 5.47 \text{ Hz}, |H(\omega)| = \frac{1}{\sqrt{1+0.029 \omega^2}}$$

$$3) f_c = 2.54 \text{ Hz}, |H(\omega)| = \frac{0.063 \omega}{\sqrt{1+3.9 \times 10^{-3} \omega^2}}$$

$$4) f_c = 510 \text{ Hz}, |H(\omega)| = \frac{1}{\sqrt{1+0.097 \times 10^{-6} \omega^2}}$$